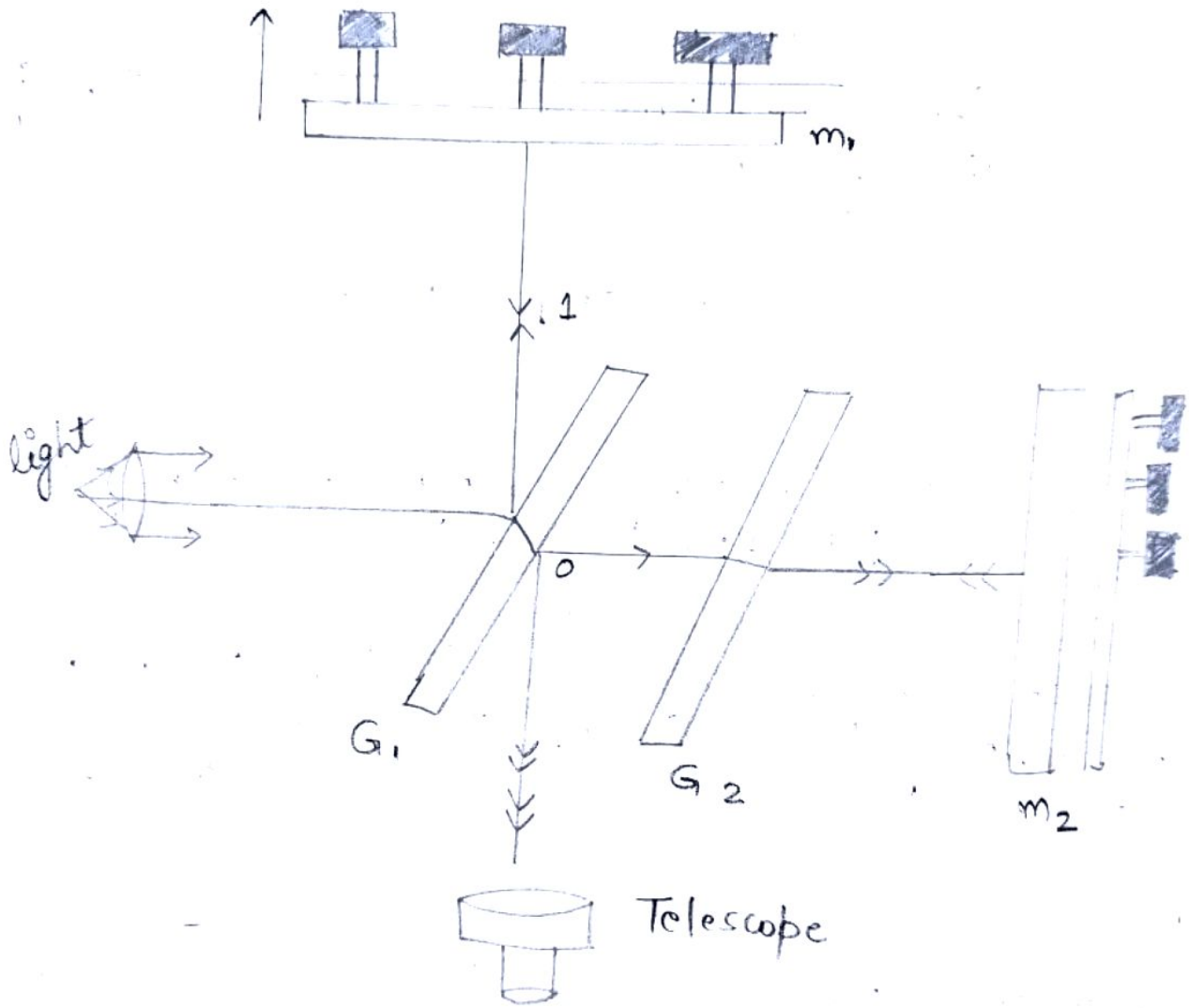


Sr. No.	Experiment	Page	E
1.	To find the wavelength of sod. light & diff. of two wavelength of Sod. light by Michelson Interferometer.		
2.	To study the operations of op. Amp		
3.	To plot output characteristics of FET and measure pinch off voltage.		
4.	To study the characteristics of Zener diode.		
5.	To plot SCR characteristic under different gate conditions.		
6.	To study Half/full wave rectifier		
7.	To study analog to digital and digit to analog conversion		
8.	Study of the characteristics of two stage R-coupled transistor amplifier.		
9.	Determine Planck's constant using solar cell and optical filter.		
10.	To determine the Planck constant with the help of photocell.		



Michelson Interferometer

Aim:- To find the wavelength of sodium light and difference of two wavelength of sodium light lines by Michelson Interferometer.

Apparatus:- Sodium lamp, Michelson Interferometer

Theory:- (i) Interference:- When two waves of same frequency, nearly same amplitude and constant initial phase difference travel in same direction along same straight lines. They superimpose in such a way that in the region of superposition the intensity is maximum at some points & minimum at some other points. This is called interference of light.

(i) Constructive Interference:- At the points where the resultant of light is maximum.

(ii) Destructive Interference:- At the points where the resultant of light (intensity) is minimum.

2. Introduction of Michelson Interferometer:-

The Michelson Interferometer first developed by Albert Michelson in 1881. has proved of vital importance in the development of modern physics. This versatile instrument was used to establish

experiment evidence for the development for the validity of the special theory of relativity to detect and measure hyperfine structure in line spectra Michelson himself pioneered of this work.

3. Adjustment of the interferometer :-

→ The distance G_1M_1 is made nearly equal to G_2M_2

→ Adjust the angle of beam splitter as needed so that the reflected beam hits the fixed mirror m_1 near its centre.

→ Adjust the angle of mirror m_1 & m_2 such that the two beams overlap on the screen.

→ The fringes initially will be very close. The no. of fringes can be increased by increasing the path difference b/w the two arms.

4. Formula used :-

(i) The wavelength λ of sodium light is given by

$$\lambda = \frac{2(x_2 - x_1)}{N} = \frac{2d}{N}$$

x_1 → initial position of the mirror m_1 ,

x_2 → final position of the mirror m_1 .

d → distance moved by mirror m_1 .

N → Number of fringes.

(ii) The difference of two wavelength of sodium lines $(\lambda_2 - \lambda_1)$ is given by-



Teacher's Signature.....

Calculations :-

(i) for wavelength of sodium light :-

Distance moved by micrometer $M_1 = \frac{D}{5} = x$

$$D = \frac{0.16 + 0.12 + 0.17 + 0.07 + 0.36 + 0.11 + 0.20 + 0.13 + 0.21 + 0.02}{10}$$

$$D = \frac{1.55}{10} = 0.155 \text{ mm}$$

$$x = \frac{D}{5} = \frac{0.155}{5} = 0.031 \text{ mm}$$

→ No. of fringes $N = 100$

$$\therefore \lambda = \frac{2x}{N} = \frac{2 \times 0.031 \times 10^{-3}}{100} = 6200 \text{ \AA}$$

$$\text{Error \%} = \frac{\text{Experiment value} - \text{standard value}}{\text{Standard value}}$$

$$= \frac{6200 - 5893}{5893} \times 100 \%$$

$$= 5.2\%$$

Expt
No.

Date

$$d_2 - d_1 = \frac{d^2_{avg}}{2X}$$

where $d^2_{avg} = d_1 d_2$

X = distance b/w the two indistinct position of mirror m_1

Observations :-

- (i) Table for wavelength of sodium light :-
least count of micrometer screw = 0.01 mm.

Table :- 1

S. No.	No. of fringes Appeared	Main scale Reading	V _R scale Reading	Table T _n (mm)	T _{n+1} - T _n = D (mm)
1.	0	0	0	0	0
2.	100	0	16	0 + 16 × 0.1 = 0.16	0.16
3.	200	0	28	0 + 28 × 0.1 = 0.28	0.12
4.	300	0	45	0 + 45 × 0.1 = 0.45	0.17
5.	400	0	52	0 + 52 × 0.1 = 0.52	0.07
6.	500	0	88	0 + 88 × 0.1 = 0.88	0.36
7.	600	0	99	0 + 99 × 0.1 = 0.99	0.11
8.	700	1	12	1 + 12 × 0.1 = 1.12	0.13
9.	800	1	32	1 + 32 × 0.1 = 1.32	0.20
10.	900	1	53	1 + 53 × 0.1 = 1.53	0.21
11.	1000	1	55	1 + 55 × 0.1 = 1.55	0.02

- (ii) Table for difference of wavelength :-
least count of micrometer screw = 0.01



Teacher's Signature

(ii) For difference of wavelength :-

Distance b/w the two indistinct position of mirror
 m_1

$$m_1 = \frac{D}{5} = \alpha \text{ (mm)}$$

$$D = \frac{1.67 + 1.31 + 1.58 + 1.64 + 1.65 + 1.60 + 1.42 + 1.53}{8}$$

$$= \frac{12.4}{8} = 1.55 \text{ mm}$$

$$\alpha = \frac{D}{5} = \frac{1.55}{5} = 0.31 \text{ mm}$$

Difference b/w two wavelength of sodium lines

$$\lambda_2 - \lambda_1 = \frac{\lambda_{avg}^2}{2x}$$

$$= \frac{(5893 \times 10^{-10} \text{ m})^2}{2 \times 0.31 \times 10^{-3} \text{ m}}$$

$$= 5.6 \text{ \AA}$$

$$\text{Error \%} = \frac{\text{Experimental value} - \text{Standard value}}{\text{Standard value}}$$

$$= \frac{5.6 \text{ \AA} - 6 \text{ \AA}}{6 \text{ \AA}} \times 100\%$$

$$= -6.67\%$$

Expt
No.

Date

S.N.	When max. intensity fringes appeared disappeared & reappeared			
	Main Scale Readings	V_R scale Readings	Total = T_n (M.S. + $V_R \times 0.1$ mm)	$T_{n+1} - T_n = D$ (in mm)
1.	0	0	0	0
2.	1	67	$1 + 67 \times 0.1 = 1.67$	1.67
3.	2	98	$2 + 98 \times 0.1 = 2.98$	1.31
4.	4	56	$4 + 56 \times 0.1 = 4.56$	1.58
5.	6	20	$6 + 20 \times 0.1 = 6.20$	1.64
6.	7	35	$7 + 35 \times 0.1 = 7.35$	1.65
7.	9	45	$9 + 45 \times 0.1 = 9.45$	1.60
8.	10	37	$10 + 37 \times 0.1 = 10.37$	1.41
9.	12	40	$12 + 40 \times 0.1 = 12.4$	1.5

Result :-(i) Wavelength of sodium light = 6200 \AA (ii) The difference of wavelength = 5.6 \AA (iii) Standard value of sodium light = 5893 \AA

Error % = 5.2%

(iv) Standard wavelength difference = 6 \AA

Error % = -6.67%

Precautions :- 1. Glass plates G_1 , G_2 & mirror M_1 , M_2 should not be touched.

2. The micrometer screw should be handle carefully.

3. The screws behind the mirror M_2 should be rotated

Teacher's Signature.....


Expt
No.

Date

through a very small angle.

4. There should not be linear or lateral displacement of circular fringes when viewed by eye.

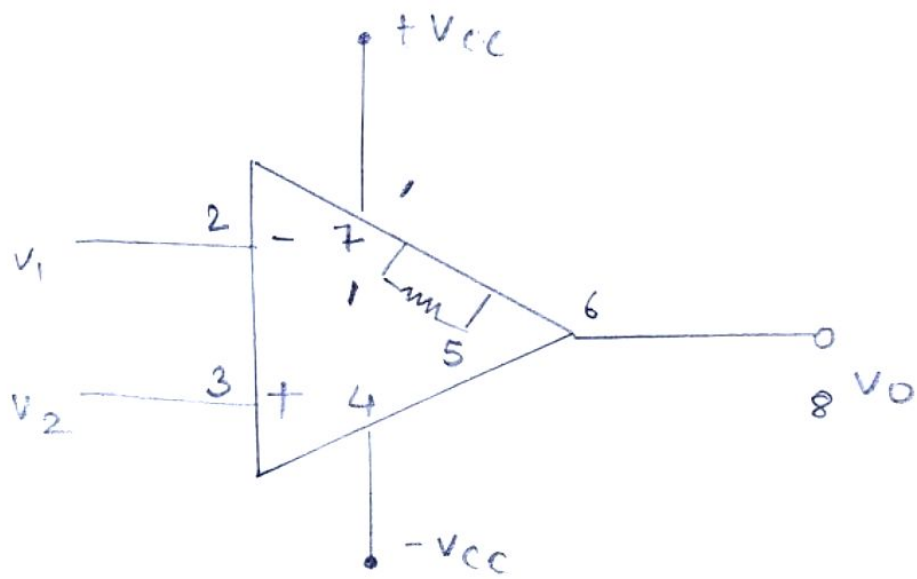5. The position of maximum indistinctness, the fringes should almost disappear.



op-amp circuit.



Aim :-

To study the operations of operational amplifier
as : 1. Inverting Amplifier
2. Non-inverting Amplifier

Apparatus :- op-Amp (741), C.R.O. (Cathode Ray oscilloscope), A.C. voltmeter & multimeter, training board of an amplifier feedback resistance.

Theory :-

Operational Amplifier :-

Op-Amp is a direct coupled high gain amplifier. This is the voltage gain op-amp differential amplifier.

Observation Table :-

Feedback resistance $R_F = 10k\Omega$ Input resistance $R_{in} = 1k\Omega$

S.No.	V_{in} (Volt)	V_o (Volt)	Voltage gain (A_v)
1.	0.1	-1	-10
2.	0.2	-2	-10
3.	0.3	-3	-10
4.	0.4	-4	-10
5.	0.5	-5	-10
6.	0.6	-6	-10
7.	0.7	-7	-10
8.	0.8	-8	-10



Teacher's Signature.....

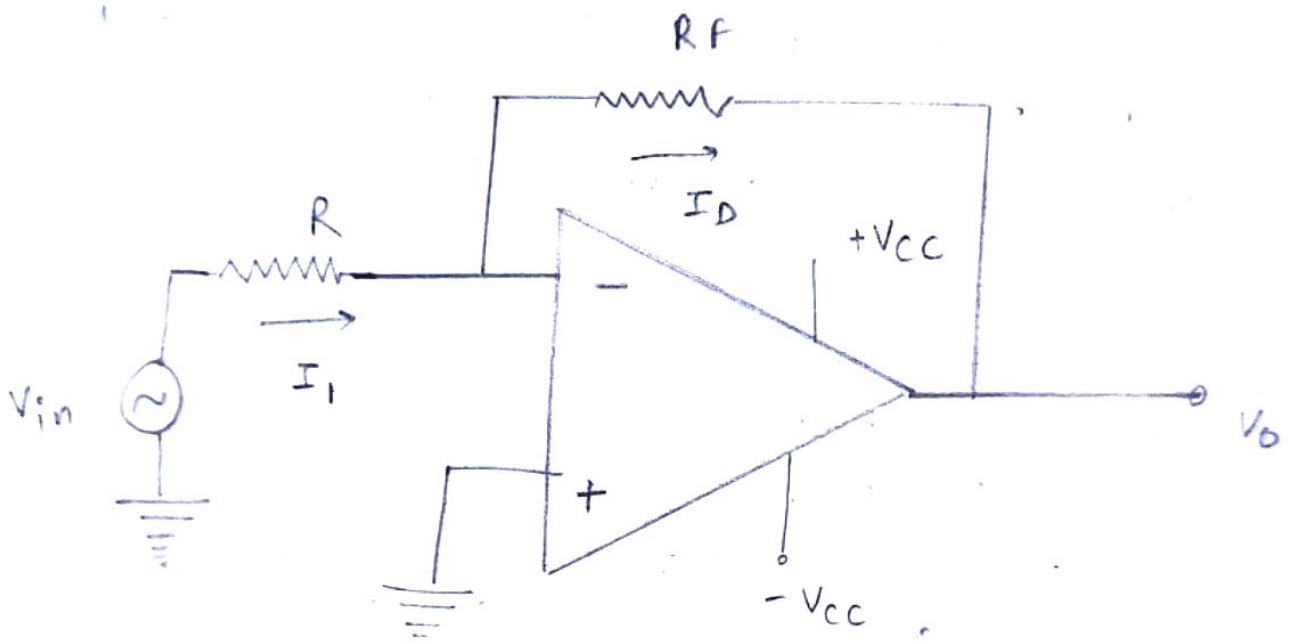


Fig:- Inverting op-amp

Expt No.				Date
9.	0.9	-9	-10	
10.	1.0	-10	-10	

The value of voltage gain A_v of op-amp is infinite. So, it produces output voltage at zero input voltage. Applying Kirchhoff's law of Node point A is $I_1 = I_2$. Due to concept of virtual ground voltage node point A is zero.

$$\frac{V_{in} - 0}{R_{in}} = \frac{0 - V_o}{R_f}$$

$$\frac{V_{in}}{R_{in}} = -\frac{V_o}{R_f}$$

$$\frac{V_o}{V_{in}} = -\frac{R_f}{R_{in}}$$

$$A_v = -\frac{R_f}{R_{in}} \quad \text{--- (1)}$$

This is the voltage gain of inverting op-amp.

Observation Table :-

Feedback resistance $R_f = 10k\Omega$

Input resistance $R_{in} = 1k\Omega$

S. No.	V_{in} (VOLT)	V_o (VOLT)	Voltage gain (A_v)
1.	0.1	-1	-10
2.	0.2	-2	-10
3.	0.3	-3	-10
4.	0.4	-4	-10

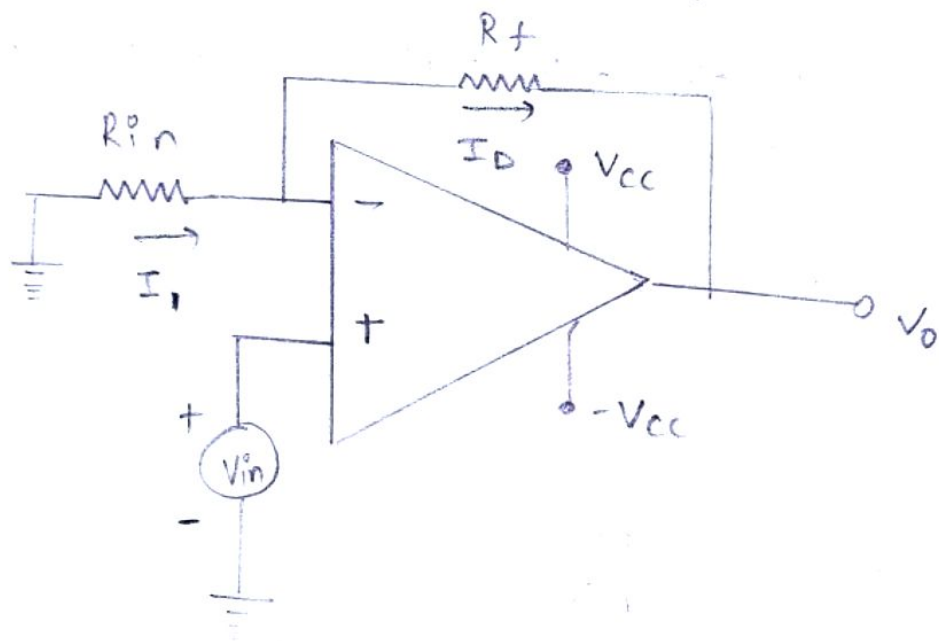


Fig :- Non-inverting Op-Amp.

5.	0.5	-5	-10
6.	0.6	-6	-10
7.	0.7	-7	-10
8.	0.8	-8	-10
9.	0.9	-9	-10
10.	1.0	-10	-10

for inverting op-amp

Theoretical & practical voltage gain are same that is

$$A_v = -\frac{R_f}{R_{in}} = -10 \text{ volt}$$

Non-inverting op-amp :-

In the circuit diagram of non-inverting feedback is added to inverting terminal from R_{in} & this terminal is grounded & we give input through the non-inverting (+) terminal

Applying Kirchoff's law at point A

$$I_1 = I_2$$

from the concept of virtual ground

$$\frac{0 - V_{in}}{R_{in}} = \frac{V_{in} - V_o}{R_f}$$

$$A_v = \frac{V_o}{V_{in}} = 1 + \frac{R_f}{R_{in}} \quad \text{--- (2)}$$

voltage gain of non-inverting op-amp is +ve i.e. output voltage & input voltage are in same phase. So, without any change of phase, we can get



Teacher's Signature.....

Expt No.

Date

sufficient gain it.

Observation Table :-

Feedback resistance $R_f = 1\text{K}\Omega$

Input resistance $R_{in} = 10\text{K}\Omega$

S.N.	V_{in} (Volt)	V_o (Volt)	Voltage gain
1.	1	1.1	1.1
2.	2	2.2	1.1
3.	3	3.3	1.1
4.	4	4.4	1.1
5.	5	5.5	1.1
6.	6	6.6	1.1
7.	7	7.7	1.1
8.	8	8.8	1.1
9.	9	9.9	1.1
10.	10	11.0	1.1

for non-inverting op-amp

Theoretical & practically voltage gain are same that is

$$A_V = 1 + \frac{R_f}{R_{in}}$$

$$= 1.1$$

Result :- 1. The observed voltage gain for inverting op-amp is equal to the theoretical voltage gain i.e. is $= -10$.

श्री

Teacher's Signature

Expt
No.

Date

2. The practical voltage gain for non-inverting op-amp is equal to the theoretical voltage gain & voltage gain is equal to 1.1.

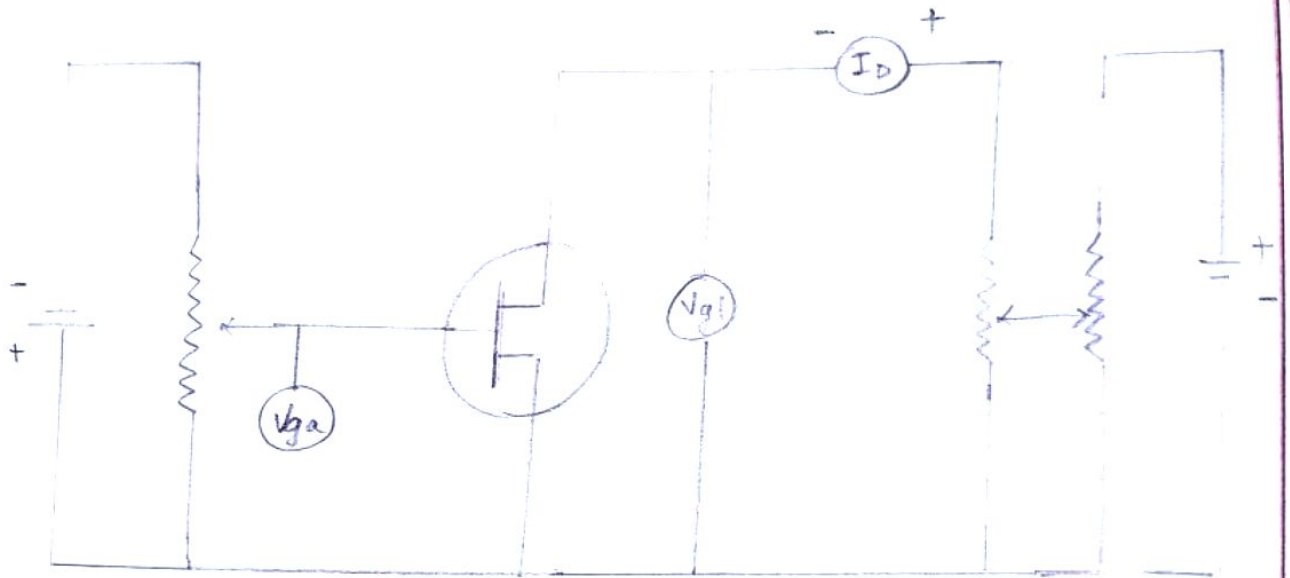


Fig: FET (Field Effect Transistor)

Expt
No. 3

Object :- To plot output characteristics of FET and measure pinch off voltage.

Apparatus :-

FET (BF w/o or BF w/e)

D.C. Voltmeter (0-30V & 0-10V) D.C.

Milimeter (0-50mA & 0-50μA)

D.C. Power supplies (for V_{GS} & V_{DS})

Circuit :- Circuit is shown in fig 1. G is gate, D is drain & source current meter I_D may have a switch to put millimeter & micrometer to the circuit (which is needed).

Procedure :- (i) Now apply V_{GS} and find 0 value for which to LC cores zero. This value of V_{GS} is called up the pinch off voltage.

(ii) Now vary V_{DS} & note I_D for a fixed value of V_{GS} . Repeat this observation for various values of V_{GS} as shown in table.

Observation :- (i) Pinch off voltage $V_p = 3.5$ volt

(ii) Table for output characteristics


No.	$V_{GS} = -1.5V$		$V_{GS} = -1.0V$		$V_{GS} = -0.8V$		$V_{GS} = -0V$	
	V_{DS}	I_D	V_{DS}	I_D	V_{DS}	I_D	V_{DS}	I_D
1.	1.2V	2.1	1.1V	1.0	1.4V	1.3	1.5V	2.1
2.	1.5V	1.3	1.8V	1.6	2.0V	2.1	2.5V	3.0

Teacher's Signature

Scale

X-axis - 1 big block

Y-axis - 1 big block

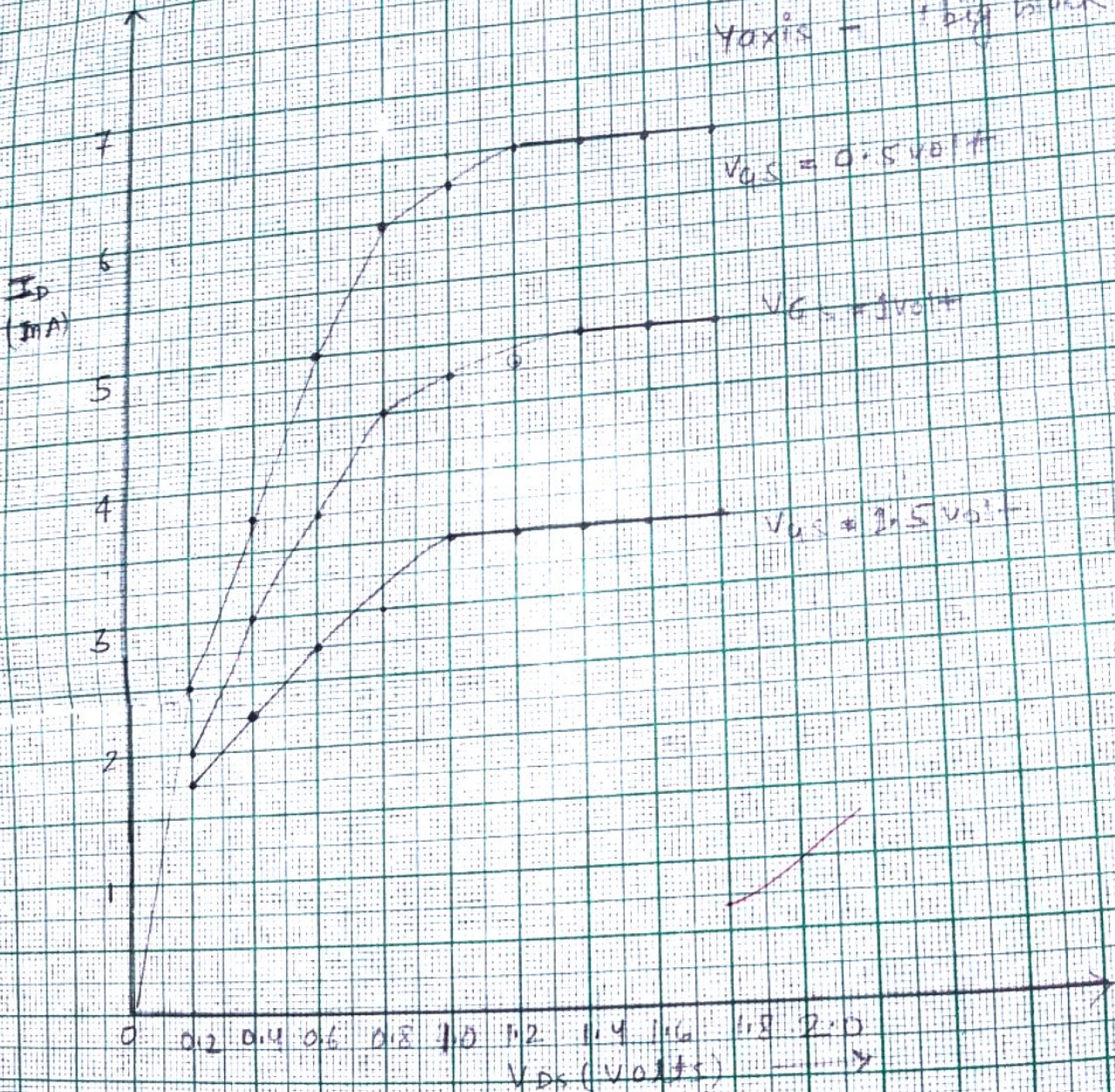


Graph b/w V_{DS} and I_D

Expt No.	Date							
3.	1.8V	1.5	2.0V	1.9	2.0V	2.25	3.0V	3.1
4.	2.0V	1.5	2.6V	2.3	2.8V	2.5	3.5V	3.2
5.	2.5V	1.6	3.0V	2.5	3.3V	2.75	4.0V	3.2

Result :- Plot a graph in V_{DS} and I_D for various value of V_{GS} . These are called output characteristics of FET.

Source of error and Precautions :-

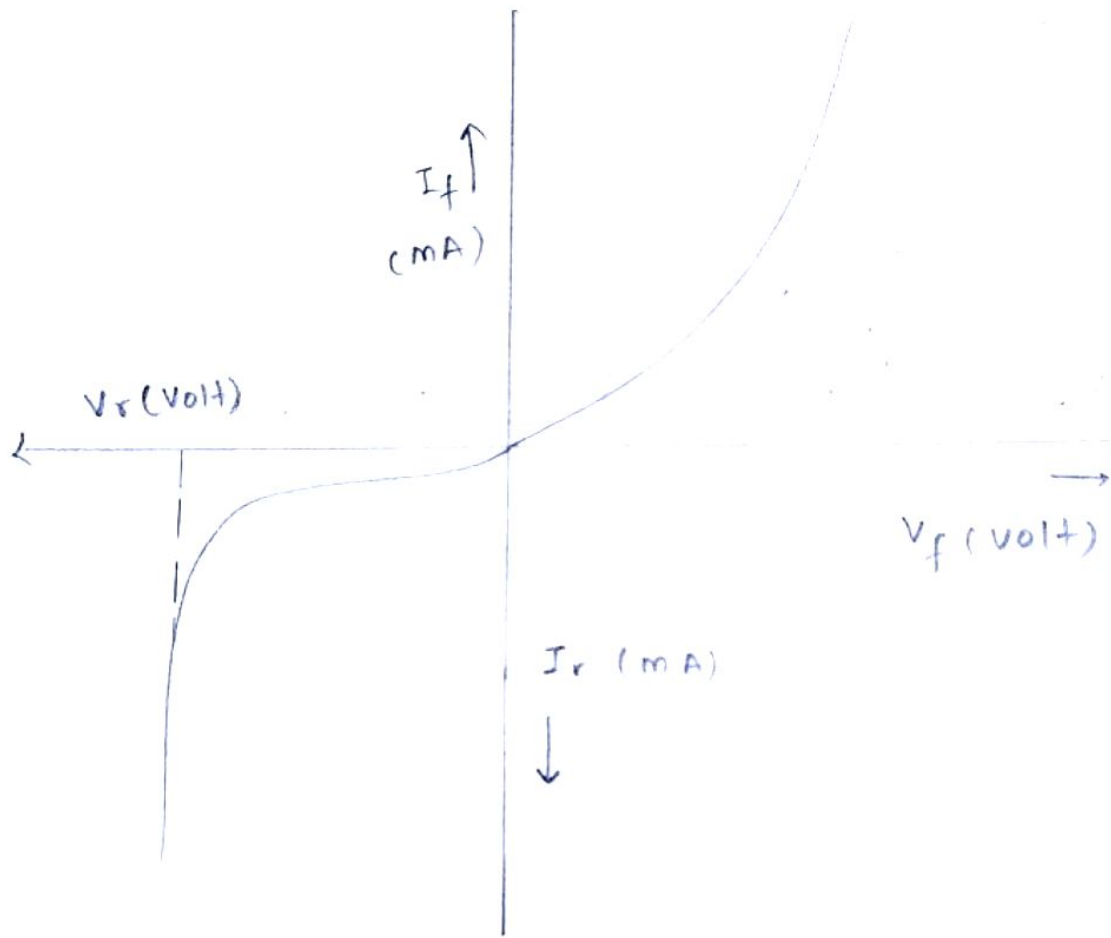1. Handle FET gently
2. Gate should never be given +ve voltage.
3. Voltage applied should not exceed the rated values.



Characteristic curve for zener diode

Object :- To study the characteristics of zener diode.

Apparatus :- Zener diode of particular rating, millimeter, voltmeter, Rheostat, connecting wire, etc.

Theory :- Zener diode is the special case of diode which permits current to flow in the forward direction but there is a difference b/w general diodes and zener diode and its as zener diode will allow to flow current in the reverse bias also they a voltage is above a certain value. This breakdown voltage is zener diode voltage.

In a standard diode. The zener voltage is high in the forward bias zener work as normal Si diode in the reverse bias.


Zener breakdown :- If both P-side and n-side of the diode are heavily doped, depletion region at the junction reduces compared to the width in normal doping. Applying a reverse bias cause a strong electric field applied across the device. As the reverse bias is \uparrow the E-field becomes strong enough to repulse covalent bond and generated large no. of charge.

for Reverse bias -


Least count for millimeter $\frac{300}{60} = 0.05 \text{ mA/div}$

Least count for voltmeter $\frac{15}{60} = 0.25 \text{ V/div}$

Teacher's Signature.....

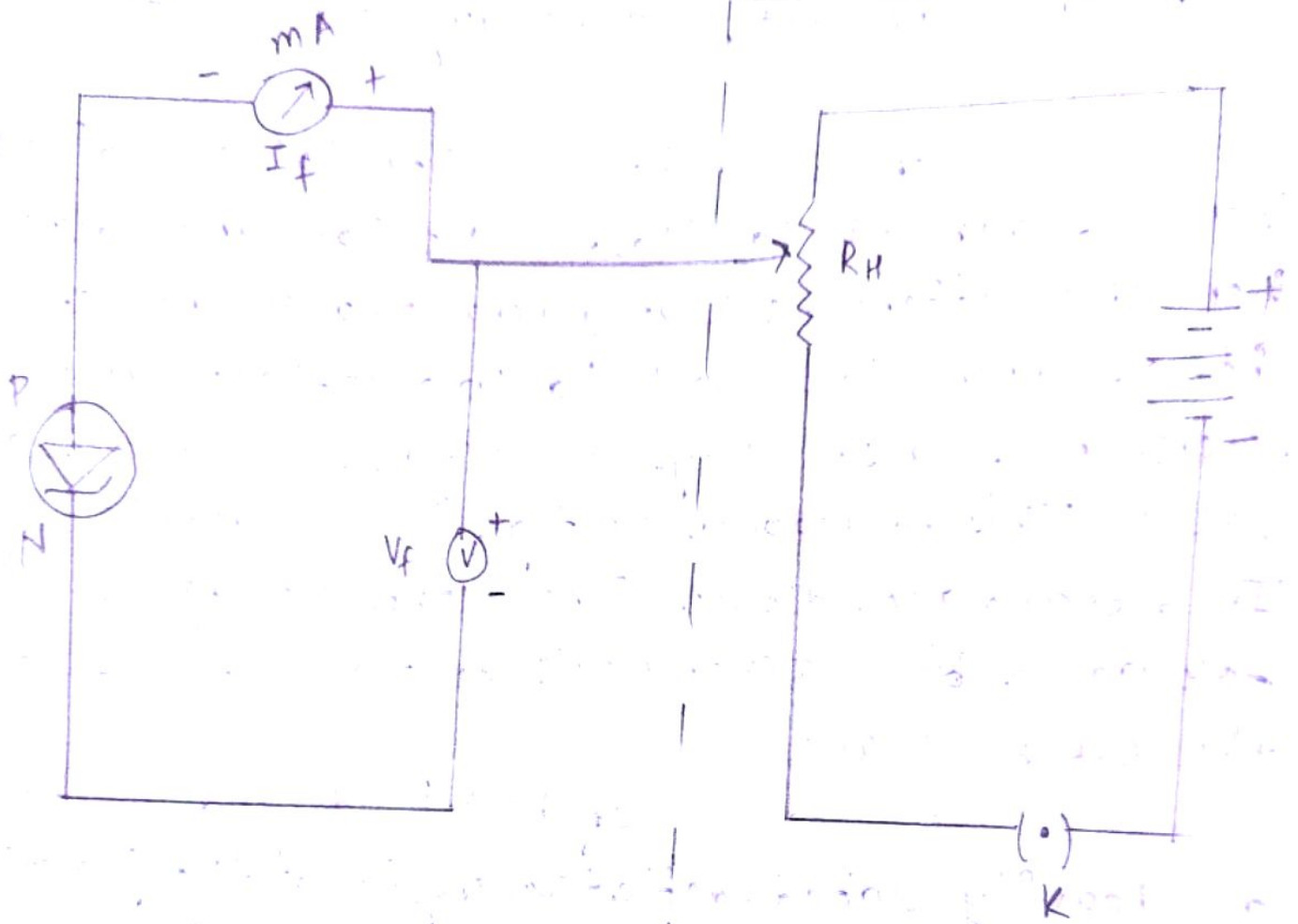


Circuit for forward bias

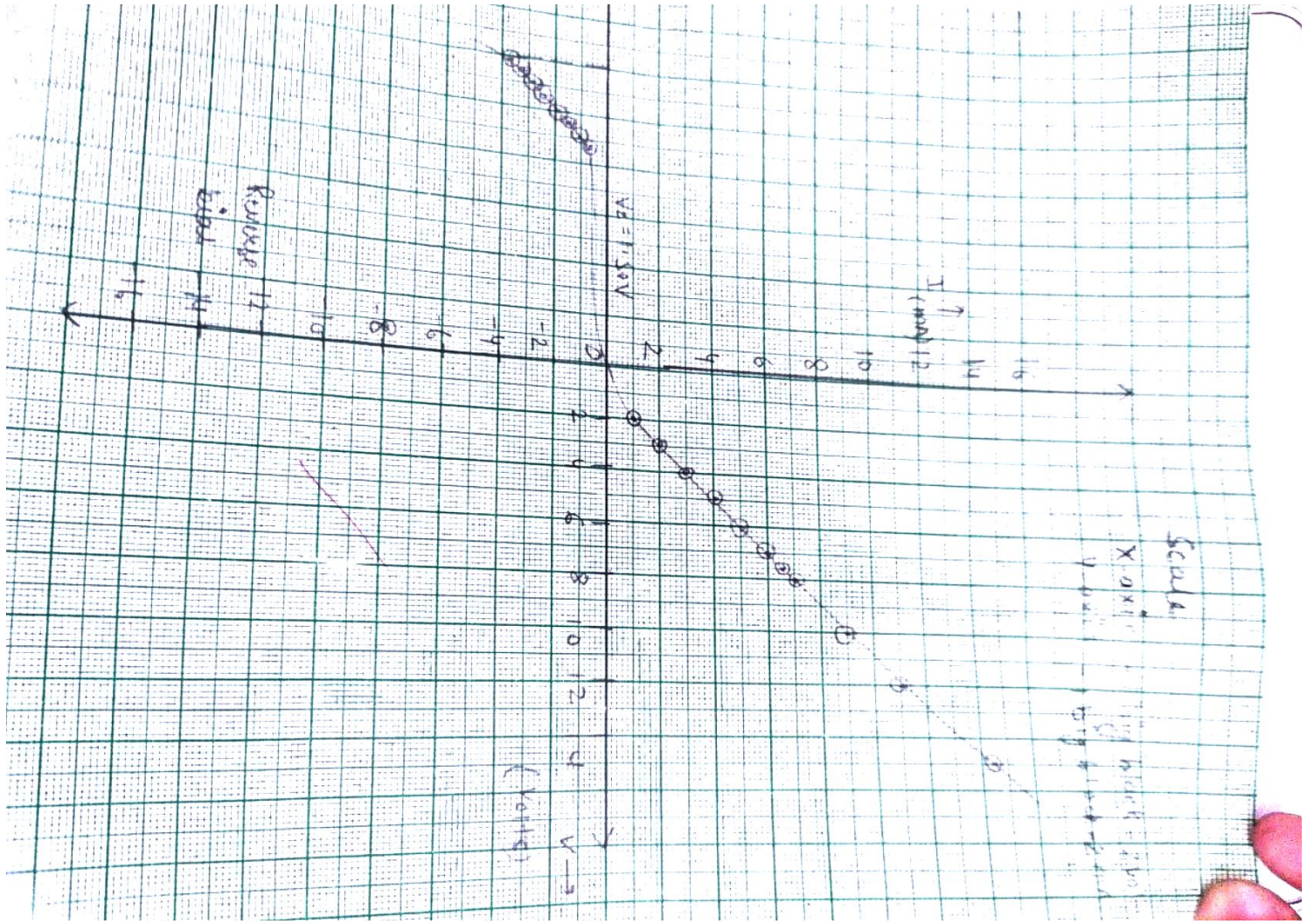


Expt No.	Reverse voltage (volts)	Current (I)
1.	8.75	0.55
2.	9.0	0.70
3.	9.25	1.0
4.	10	1.70
5.	10.5	2.05
6.	10.75	2.4
7.	11	2.65
8.	11.25	2.85
9.	11.50	3.0
10.	9.75	1.15

Results :- Graphs plotted b/w current and volt and with help of this we get Zener diode. $V_Z = 11.5$ volt.

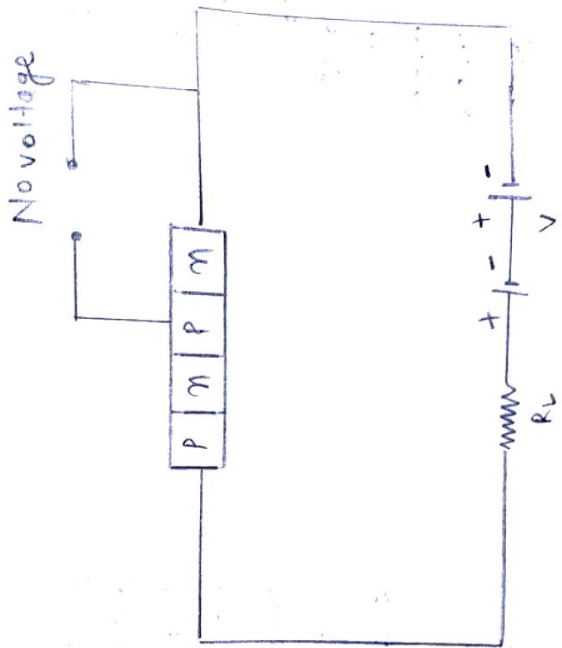Precautions - In the state of forward bias voltage must be change through small values and the value of current due to \uparrow voltage should not exceed the max. allowed for diode.



When Gate is OFF

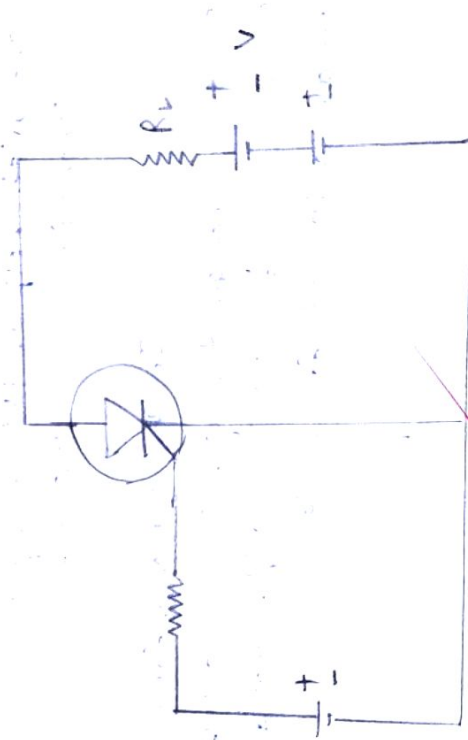

When Gate is ON

Object :- To plot SCR characteristic under different gate conditions.

Apparatus - 1) Two continuous variable DC regulated power supplies of 0.5 and 0-30V.

2) Three meters to measure voltage and current mounted on front of panel and connections on 4mm² sockets.

3) SCR (2-6CM) placed outside the cabinet and connections are brought out of sockets.

Theory :- SCR is a three terminal device SCR are used as a controlled switch. It is a uni-directional power switch. In SCR load is connected in series with anode. The anode is always kept +ve with respect to cathode. The working of SCR can be studied under the following steps -

When gate is open :-

Gate is open that is no voltage is applied to the gate under this condition Junction J_1 is reverse biased while Junctions J_1 and J_2 are forward biased no current flow through J_1 and the SCR is cutoff. If the applied voltage is a stage is reached when reverse biased junction J_2 breaks down. The SCR now conducts heavily and said to be unstable.

Breakdown voltage :- applied voltage at which SCR conducts heavily without gate voltage.

No.


When gate is positive with respect to cathode:-
SCR can be made to conduct heavily at smaller applied voltage small + potential to the gate J_3 is forward bias and J_2 is reverse biased and gate current starts following as soon as gain current flows, an current I_4 entering small time, J_2 break down and SCR starts conducting. The gate loss at controls every if gate voltage is removed. The anode current do not decrease at all. The only way to be SCR in off condition is to reduce the applied voltage are zero.

Peak reverse voltage:- Maximum reverse voltage that can be applied to an SCR without conducting in the reverse condition.

Holding current:- Maximum anode current gate being open at which SCR is turned off from on conditions

Observations:- least count voltage = 0.5 V/div .
least count of millimeter 0.02 V/div

When gate is off (that $I_g = 0$)

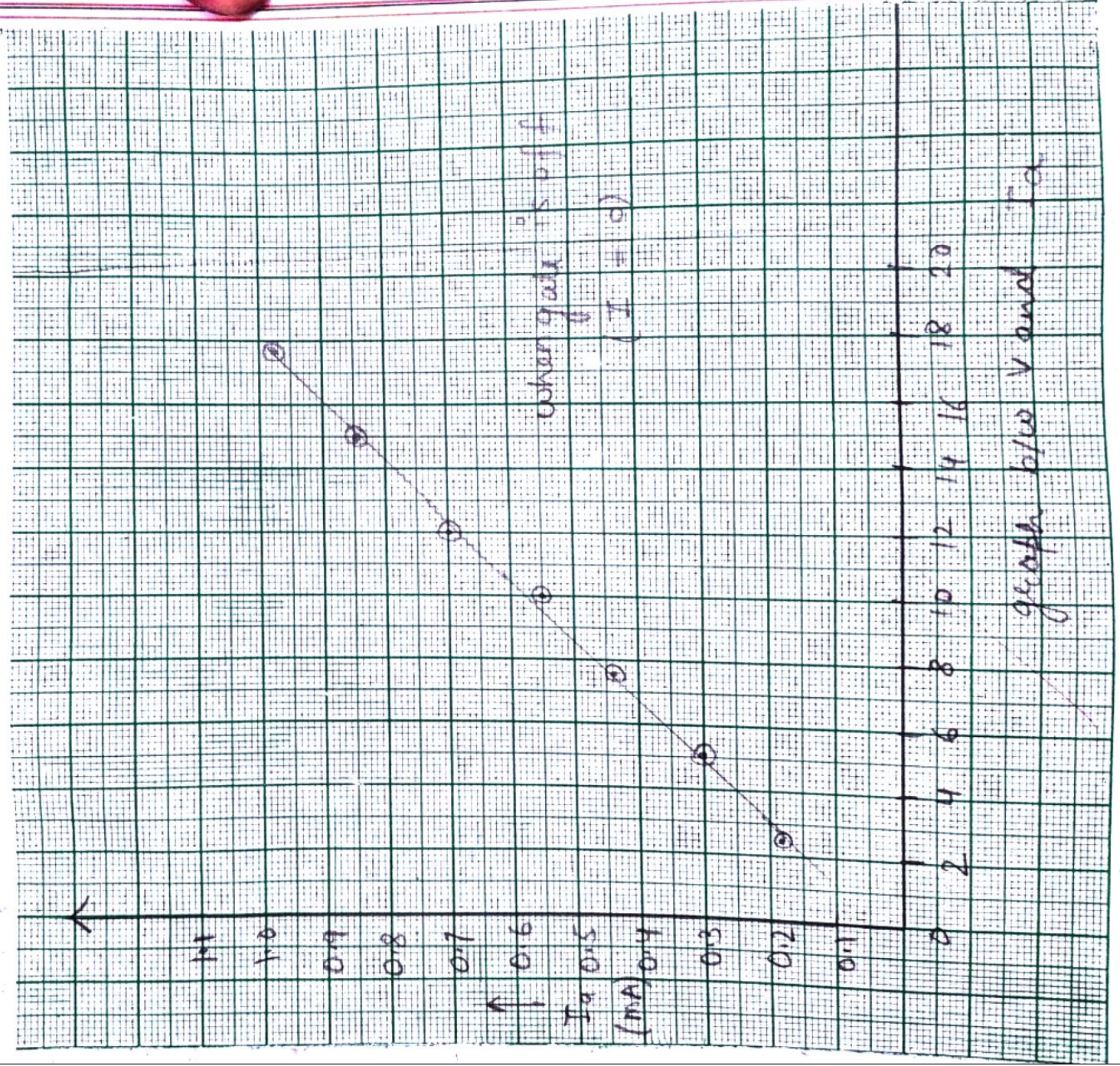

Sr. No.	V_g (Volt)	I_a (mA)
1.	0	0.04
2.	2.5	0.18
3.	5.0	0.30
4.	7.5	0.44
5.	10.0	0.56
6.	12.5	0.70
7.	15.0	0.84
8.	17.5	0.98
9.	20.0	1.10

Results: - A Graph is drawn b/w I_a and V_g for various gate voltages and thus we get SCR characteristics.

Precautions :-

1. SCR should not be operated in the Avalanche breakdown region because SCR is a unidirectional device.
2. SCR must be held gently.


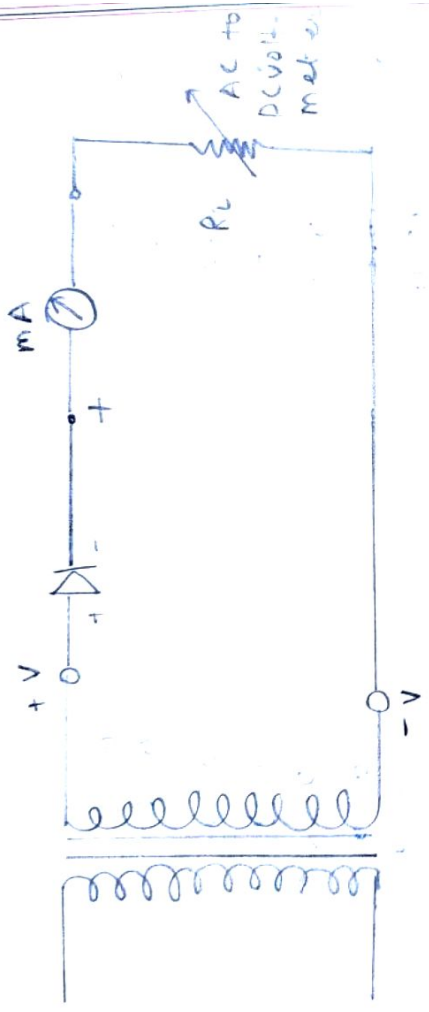


Fig. Half wave rectifier

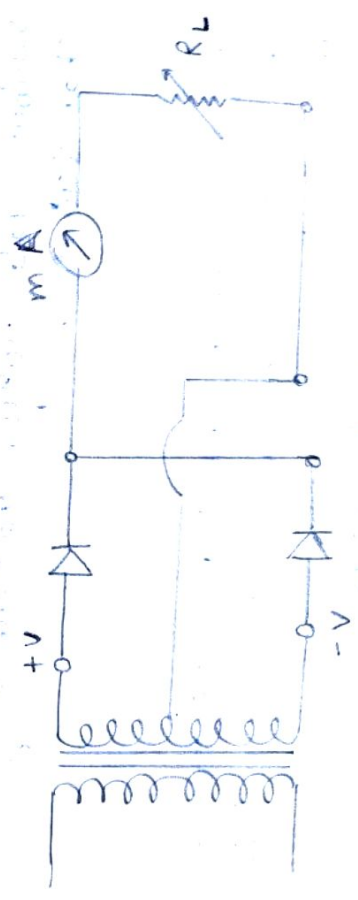

Full wave rectifier

Object:- To study Half/Full wave rectifier

Apparatus:- New tech electronic training board

type NTI-112

VIVM (vacuum tube voltmeter) or

AC voltmeter.

Theory:- The ripple factor (r) of a power supply percentage is defined as

$$r = \frac{V_{ac}}{V_{dc}} \times 100\%$$

where r = ripple factor at given load

V_{ac} = AC output voltage

V_{dc} = DC output voltage

In electronic devices operation DC voltages and currents are required so the process by which AC is converted into DC is known as rectification. The process when a diode conducts during either positive or negative half of input cycle is called Half wave rectification.

When two rectifiers are used with a center tapping transformer full wave rectification is obtained. There two diodes D_1 and D_2 alternatively conduct in two alternations of input sin wave.

Calculation :-

Set 1st :- for Half wave rectifier \rightarrow Ripple factor (λ)
 $= \frac{V_{ac}}{V_{dc}}$

(i) $R_L = 1\Omega, V_{DC} = 2V, I_L = 200mA, V_{AC} = 2V$

$\lambda = \frac{2}{2} = 1$

(ii) $R_L = 2\Omega, V_{DC} = 3.2V, I_L = 60mA, V_{AC} = 3.8V$

$\lambda = \frac{3.8}{3.2} = 1.1875$

(iii) $R_L = 3\Omega, V_{DC} = 4.0V, I_L = 140mA, V_{AC} = 5.0V, r = \frac{5}{4}$

(iv) $R_L = 4\Omega, V_{DC} = 4.6V, I_L = 120mA, V_{AC} = 5.8V, r = \frac{5.8}{4.6} = 1.26$

(v) $R_L = 5\Omega, V_{DC} = 5V, I_L = 100mA, V_{AC} = 6.4V, r = \frac{6.4}{5} = 1.28$

(vi) $R_L = 6\Omega, V_{DC} = 5.4V, I_L = 90mA, V_{AC} = 7.0V, r = \frac{7}{6.4} = 1.09$

(vii) $R_L = 7\Omega, V_{DC} = 5.8V, I_L = 80mA, V_{AC} = 7.4V, r = \frac{7.4}{5.8} = 1.275$

(viii) $R_L = 8\Omega, V_{DC} = 6.0V, I_L = 70mA, V_{AC} = 7.8V, r = \frac{7.8}{6.0} = 1.3$

Ripple factor of half wave rectifier

$\lambda = 1 + 1.1875 + 1.25 + 1.28 + 1.29 + 1.275 + 1.3$

8

$\lambda = 1.2303$

theoretical value = 1.21

% error = $\frac{Th - Pr}{Th} \times 100\% = 1.67\%$

Expt No.

Observation:- least count of Vdc voltmeter = 0.2 volt
 least count of Vac voltmeter = 0.2 vo
 least count of load current (Iac) = 5mA

Operation table:- For Half wave rectifier:-

S.No	Load resistance	DC/ff voltage (V)	least current I _L (mA)	Vac (V)	Ripple factor $r = \frac{V_{ac}}{V_{dc}}$
1		2	200	2	1
2		3.2	160	3.8	1.1875
3		4.0	140	5.0	1.25
4		4.6	120	5.8	1.260
5		5.0	100	6.4	1.28
6		5.4	90	7.0	1.29
7		5.8	80	7.4	1.275
8		6.0	70	7.8	1.3

For full wave rectifier

S.No	Load Resistance (R _L)	DC voltage	load current I _L (mA)	Vac (V)	Ripple factor $r = \frac{V_{ac}}{V_{dc}}$
1	1	3.2	250	1.8	0.5625
2	2	4.8	240	2.4	0.50
3	3	6.2	210	3.6	0.5806
4	4	6.8	170	3.8	0.5588
5	5	7.2	140	4.0	0.555

Set 2nd

For full wave rectifier - Ripple factor (r) = $\frac{V_{ac}}{V_{dc}}$

(i) $R_L = 1\Omega$, $V_{DC} = 8.2V$, $I_L = 2.50mA$, $V_{ac} = 1.8V$
 $r = \frac{V_{ac}}{V_{DC}} = \frac{1.8}{8.2}$

(ii) $R_L = 2\Omega$, $V_{DC} = 4.8V$, $I_L = 240mA$, $V_{ac} = 2.4V$, $r = \frac{2.4}{4.8} = 0.5$

(iii) $R_L = 3\Omega$, $V_{DC} = 6.2V$, $I_L = 210mA$, $V_{ac} = 3.6V$, $r = \frac{3.6}{6.2} = 0.5806$

(iv) $R_L = 4\Omega$, $V_{DC} = 8.8V$, $I_L = 170mA$, $V_{ac} = 3.8V$, $r = \frac{3.8}{8.8} = 0.5588$

(v) $R_L = 5\Omega$, $V_{DC} = 7.2V$, $I_L = 140mA$, $V_{ac} = 4.0V$, $r = \frac{4.0}{7.2} = 0.555$

(vi) $R_L = 6\Omega$, $V_{DC} = 7.6V$, $I_L = 128mA$, $V_{ac} = 4.2V$, $r = \frac{4.2}{7.6} = 0.5526$

Ripple factor for full wave rectifier

$$r = \frac{0.5625 + 0.50 + 0.5806 + 0.5588 + 0.55}{6} = 0.5526$$

Theoretical value = 0.55075

$$\% \text{ error} = \frac{Th - Pr}{Th} \times 100\% = \frac{0.55075 - 0.5526}{0.55075} \times 100 = -1.478\%$$

Expt
No.

Date

6

6

7.6

12.5

4.2


0.5526

Results :-

Ripple counter for \rightarrow

(i) half wave rectifier $\rightarrow 1.2303$

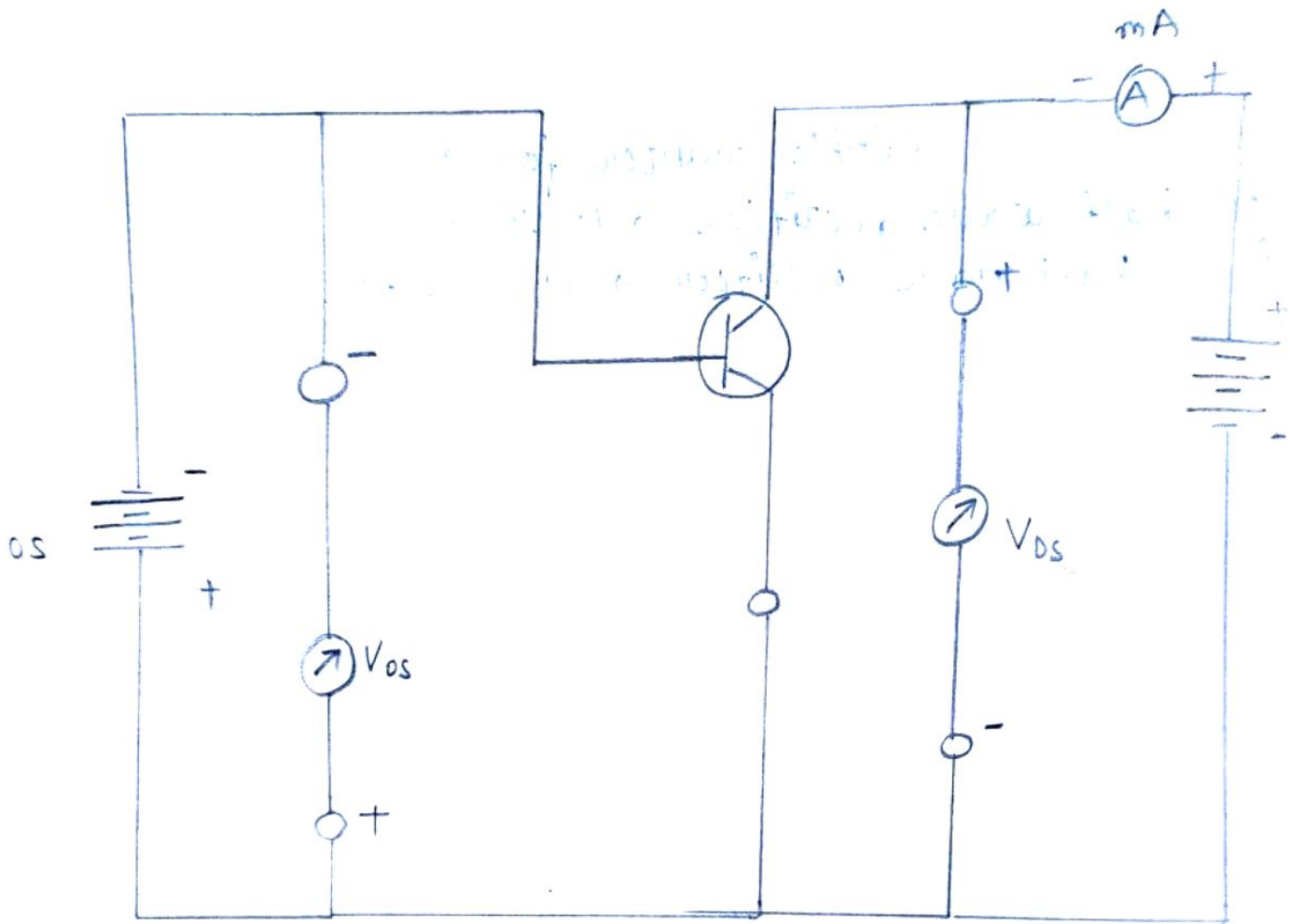(ii) full wave rectifier $\rightarrow 0.55075$



Object:- To study analog to digital and digital to analog conversion.

Apparatus:- Analog to digital converter panel board, connecting wires.

Theory :- The data in a processor is in digital terms. This different beam of outside is used where data this analog form to get digital data form.

We need to use the analog to digital it converts analog voltage word after an A/D has proceed dai answer into and analog voltage or the conversion a D/A conversion.

Observation Table :-

(A) For D/A converter -

S.No.	I/P Digital Signal				Calculated o/p (volt)	Observed voltage (V)	Calculated o/p voltage
	2^0 A	2^1 B	2^2 C	2^3 D			
1	0	0	0	0	0	0.26	0
2	1	0	0	0	0.33	0.56	1
3	0	1	0	0	0.66	0.86	2
4	1	1	0	0	1.0	1.16	3
5	0	0	1	0	1.33	1.43	4
6	1	0	1	1	1.66	1.73	5
7	0	1	1	0	2.0	2.03	6

Expt No.		Date	
----------	--	------	--

8	1	1	1	0	2.33	2.33	7
9	0	0	0	1	2.66	2.66	8
10	1	0	0	1	3.0	2.90	9
11	0	1	0	1	3.33	3.20	10
12	1	1	0	1	3.66	3.50	11
13	0	0	1	1	4.0	3.78	12
14	1	0	1	1	4.33	4.08	13
15	0	1	1	1	4.66	4.39	14
16	1	1	1	1	5.0	4.70	15

For A/D converter -

S.No	Analog i/p Voltage	Digital o/p voltage	7-segment display
		$2^0 2^1 2^2 2^3$	
1	0	0 0 0 0	111
2	1	1 0 0 0	1
3	2	0 1 0 0	2
4	3	1 1 0 0	3
5	4	0 0 1 0	4
6	5	1 0 1 0	5
7	6	0 1 1 0	6
8	7	1 1 1 0	7
9	8	0 0 0 1	8
10	9	1 0 0 1	9
11	10	0 1 0 1	10
12	11	1 1 0 1	11

INU.									
13	18	0	0	1	1				13
14	13	1	0	1	1				13
15	14	0	1	1	1				14
16	15	1	1	1	1				15

RESULT :- A/D converter \rightarrow we get digital o/p as shown in the table.

D/A converter \rightarrow we get analog o/p of digit input in table.

PRECAUTIONS :- (i) Keep the circuit switched off while not taking any it may damage circuit.
 (ii) Note readings carefully.

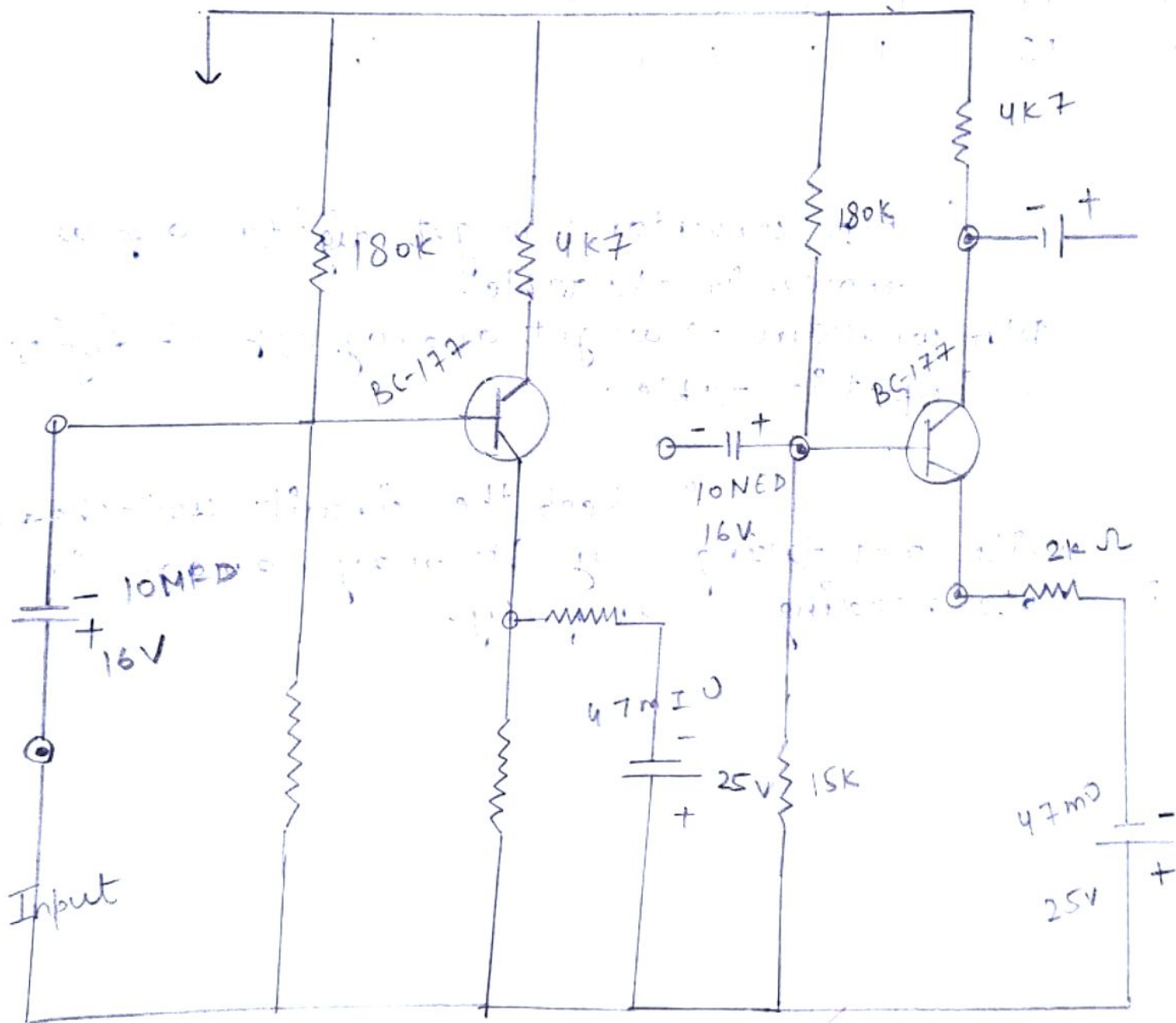


Fig - RC - coupled transistor amplifier

Object:- Study of the characteristic of two stage R-C coupled transistor Amplifier.

Study of the frequency response of the Individual as well as R-C coupled Amplifier.

Apparatus:-

OMG 0 - Type ETB-45 experiment at training Board two PNP transistor AC millimeter cathode ray oscilloscope main ON/OFF switch phone.

INTRODUCTION:- This is the most popular type of coupling because it's cheap & provides excellent audio frequency (because of) fidelity over a wide range of frequency. It is usually employed for voltage amplification fig(1) shows two stage of an R-C coupled amplifier.

Circuit Description:- Since fig(1) shows two stage of an R-C-coupled amplifier A coupled capacitor C_c is used to connect the output of the first stage to the base (i.e. input) of the 2nd stage. It is so on the resistance R_1 , R_2 & R_E form the biasing & stabilisation network. The emitter by pass capacitor. A low resistance path to the signal without it. The voltage gain of each stage would be lost. The coupling capacitor C_c transit AC signal but block DC. This prevent DC interference b/w various stage and the shifting

Teacher's Signature.....

Calculations :-

$$\begin{aligned} \text{Current} &= 2 \text{ mA (constant)} \\ \text{distance b/w probes} &= 0.9 \text{ cm} \\ \text{thickness of crystals} &= 0.05 \text{ cm} \end{aligned}$$

1) For the given sample $\left(\frac{\omega}{89}\right) = \frac{0.05}{0.2} = 0.25$

2) The correction factor $= \frac{25}{\omega} \log 2$

$$= \frac{2 \times 0.2 \times 2.303 \times 0.3010}{0.05}$$
$$= 5.54$$

At temp $32^\circ \text{C} = 305 \text{ K}$

$$\frac{10^3}{T} = \frac{10^3}{30} = 328$$

$I = 2 \text{ mA}$; $V = 89.35 \text{ mV}$; $e = \frac{V}{I} = \frac{35}{2 \left(\frac{\omega}{s}\right)}$

$$\begin{aligned} \rho &= \frac{78.6 \times 2 \times 1.314 \times 0.2}{5.54} \\ &= 786 (0.326) \\ &= 17.29 \text{ } \Omega \text{ cm} \end{aligned}$$

Similarly it calculates for all temp & slope b/w 10^3 & $\log e$ is

$$= \frac{1.10 - 1.05}{2.75 - 2.72} = \frac{0.05}{0.03} = 1.66 \text{ cm}$$

Energy gap $E_g = 2.303 \times 10^3 \times 2 \text{ K} \times \text{slope}$

of operation.

When AC signal is applied to the base of the first transistor it is amplified. In the first stage, the amplified signal is developed across its collector load R_C . The amplified signal is then given to the base of the next stage through a coupling capacitor C_C . The 2nd stage does further amplification of the signal. In this way, the cascaded connection of two or more stages amplifies the signal & the overall gain is considerably increased.

It may be that the total gain is less than the product of the gains of individual stages. This is because when a 2nd stage is made to follow the first stage, the effective load resistance of the first stage is reduced due to the shunting effect of the input resistance of the 2nd stage. This reduces the gain of the stage which is loaded by the next stage.

Observation table:-



S.No.	Frequency	V_i (V)	V_o (V)	Gain $A_p = V_o/V_i$
1.	23.3 Hz	$2.6 \times 50 \text{ mV} = 0.13 \text{ V}$	$1.6 \times 0.2 \text{ V} = 0.32 \text{ V}$	2.4
2.	40.72 Hz	0.13 V	$1.8 \times 0.2 \text{ V} = 0.36 \text{ V}$	2.7
3.	81.00 Hz	0.13 V	$2 \times 0.2 \text{ V} = 0.4 \text{ V}$	3.01
4.	140.2 Hz	0.13 V	$2.2 \times 0.3 \text{ V} = 0.44 \text{ V}$	3.3
5.	221.6 Hz	0.13 V	$2.4 \times 0.2 \text{ V} = 0.48 \text{ V}$	3.692

Teacher's Signature

Expt No.				Date
6.	506.6	0.13 V	$2.4 \times 0.2 = 0.48V$	3.692
7.	1 KHz	0.13 V	$2.4 \times 0.2 = 0.48V$	3.692
8.	2 KHz	0.13 V	$2.4 \times 0.2 = 0.48V$	3.692
9.	10 KHz	0.13 V	$2.4 \times 0.2 = 0.48V$	3.692
10.	12 KHz	0.13 V	$2.4 \times 0.2 = 0.48V$	3.692
11.	14 KHz	0.13 V	$2.2 \times 0.2 = 0.44V$	3.38
12.	15 KHz	0.13 V	$2.2 \times 0.2 = 0.44V$	3.38
13.	16 KHz	0.13 V	$2 \times 0.2 = 0.38V$	3.07
14.	18 KHz	0.13 V	$2 \times 0.24 = 0.38V$	2.92
15.	23.56 KHz	0.13 V	$1.8 \times 0.2 = 0.36V$	2.76
16.	26 KHz	0.13 V	$1.6 \times 0.2 = 0.32V$	2.46
17.	30 KHz	0.13 V	$1.4 \times 0.2 = 0.28V$	2.30
18.	34 KHz	0.13 V	$1.4 \times 0.2 = 0.28V$	2.15
19.	40 KHz	0.13 V	$1.2 \times 0.2 = 0.24$	1.846

Result:- From the graph we see that

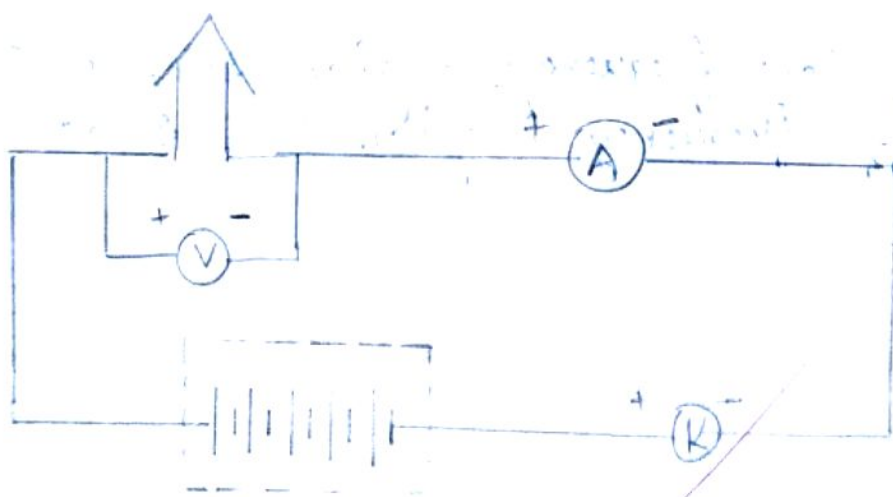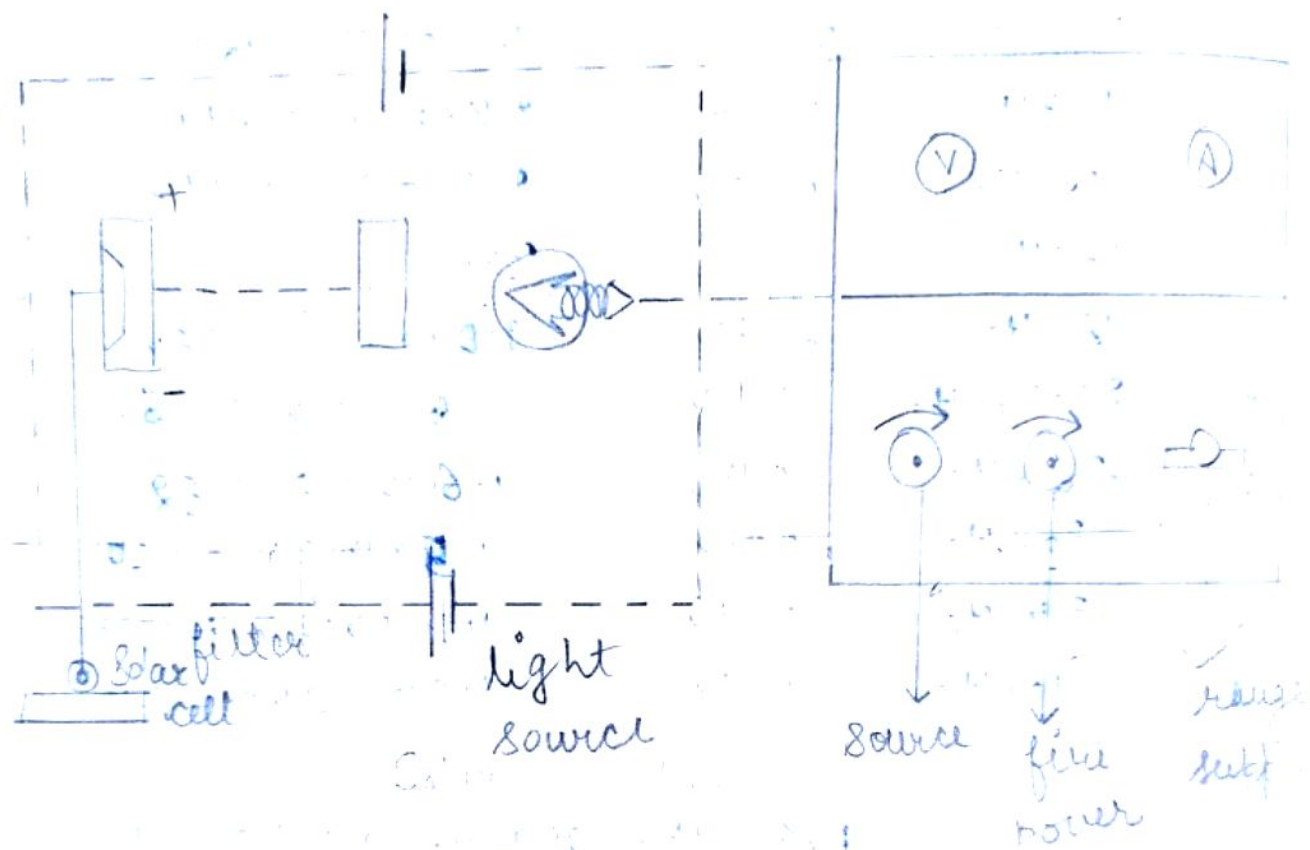- (i) The cut off low frequency region 3.69 at 506.6 Hz
- (ii) High cut off frequency region 3.692 at 1200 Hz or 12 KHz



Circuit diagram

Object:- Determine Planck's constant using solar cell and optical filter.

Apparatus:- The new tech type board EM 102 is contact. It comprises a DC micrometer, DC vol. Three knobs coarse fine range one LED & ON. Blue, Red, green filter, is

Theory:- For Black body energy distribution is given

$$E_{\lambda} d\lambda = \frac{8\pi hc}{\lambda^5} \exp\left(-\frac{hc}{\lambda T}\right) d\lambda$$

where $E_{\lambda} d\lambda$ is total energy radiated by black body to $\lambda + d\lambda$ interval.

$h \rightarrow$ plank constant

$c \rightarrow$ Velocity of light

$T \rightarrow$ Absolute temp.

$k \rightarrow$ Boltzmann factor

According to wein's formula

$$E_{\lambda} = \frac{8\pi hc}{\lambda^5} e^{-hc/\lambda T} \quad \text{--- (1)}$$

Taking loge of eqⁿ (1)

$$\ln E_{\lambda} = \ln A - \frac{\ln hc}{\lambda KT}$$

we know energy radiated directly proportional to photo

$$E_{\lambda} \propto \theta$$

$$\ln E_{\lambda} = \ln A + \ln \theta \quad \text{--- (2)}$$

Calculations :-

i) for first and second filter

$$h_1 = \frac{e(V_2 - V_1) d_1 d_2}{c(\lambda_1 - \lambda_2)} \text{ J-sec}$$

$$h_1 = \frac{1.6 \times 10^{-19} \times (V_2 - V_1) \times 6143 \times 5645 \times 10^{-20}}{3 \times 10^8 \times 498 \times 10^{-10}}$$

$$h_1 = 37.14 (V_2 - V_1) \times 10^{-34}$$
$$= 37.14 \times (2.20 - 1.98) \times 10^{-34} = 8.17 \times 10^{-34}$$

$$\boxed{h_1 = 8.17 \times 10^{-34} \text{ J-sec}}$$

ii)

for second and third filter.


$$h_2 = \frac{e(V_3 - V_2) d_2 d_3}{c(\lambda_2 - \lambda_3)} \text{ J-sec}$$

$$h_2 = \frac{1.6 \times 10^{-19} (V_3 - V_2) 5645 \times 4865 \times 10^{-20}}{3 \times 10^8 \times 780 \times 10^{-10}}$$

$$h_2 = 18.78 (V_3 - V_2) \times 10^{-34}$$


$$\boxed{h_2 = 15.02 \times 10^{-34} \text{ Joule-sec}}$$

for Blue colour filter

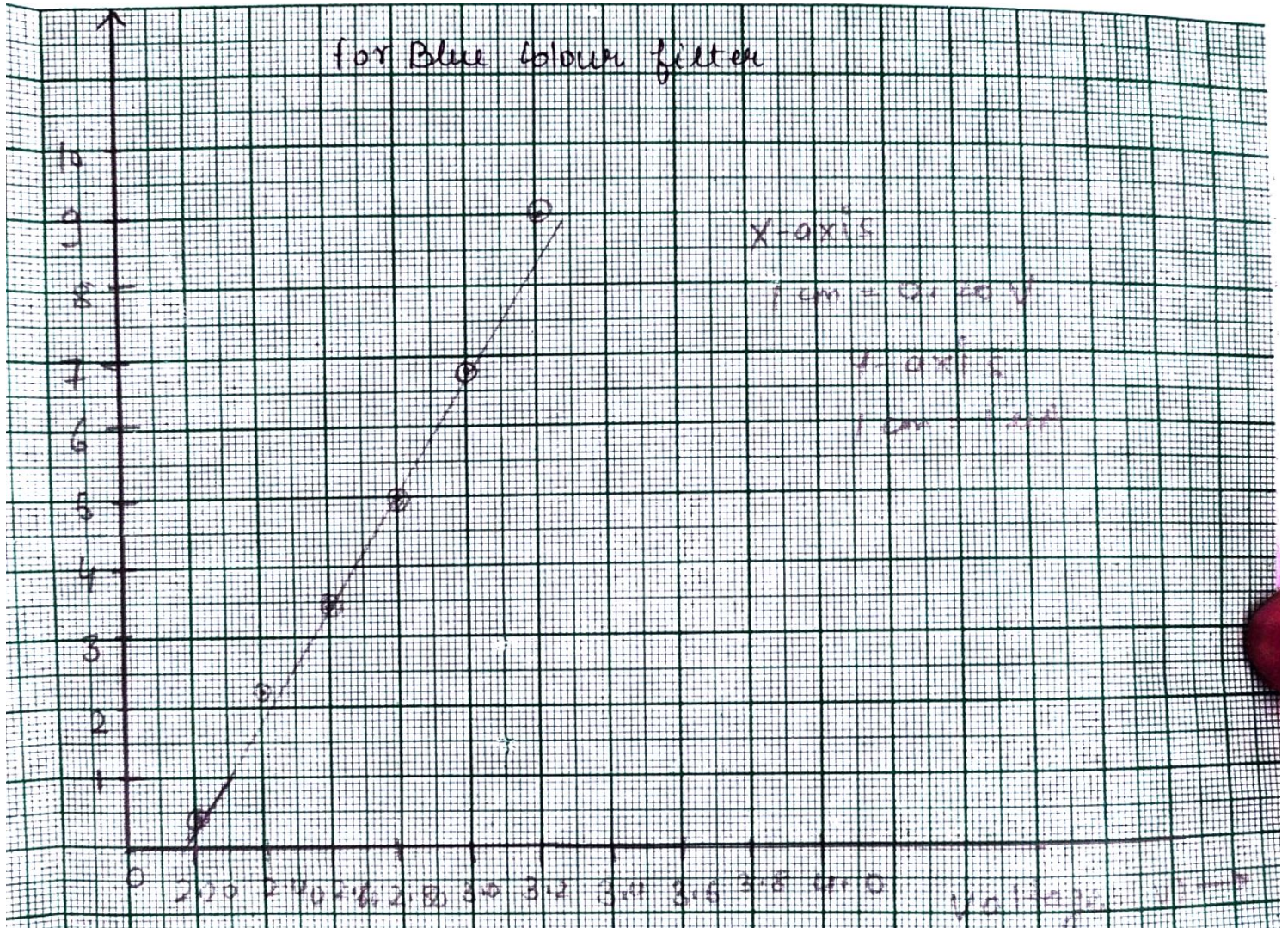

for Red filter

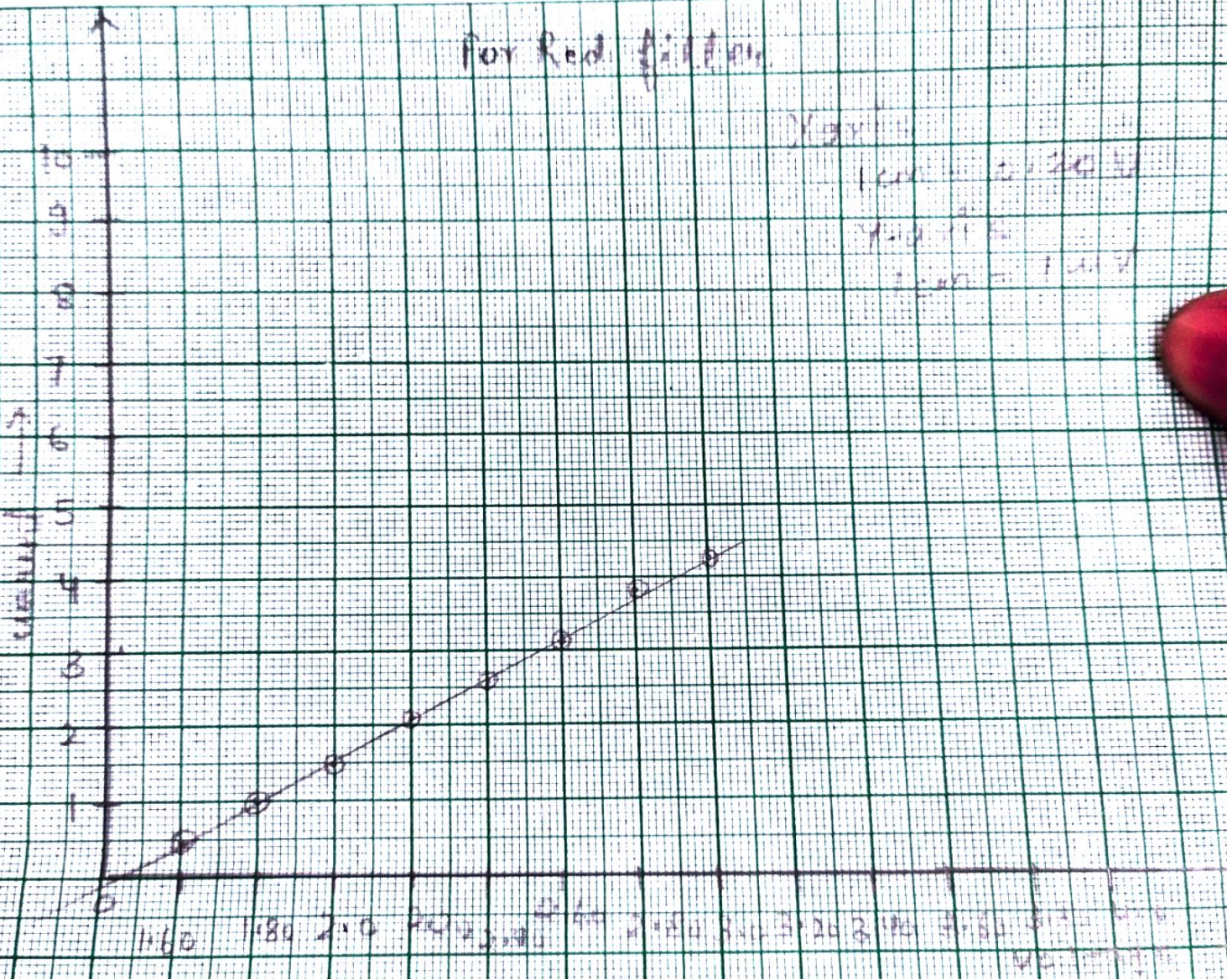Mean
 $\frac{1.60 + 1.80 + 2.00 + 2.20 + 2.40 + 2.60 + 2.80 + 3.00 + 3.20 + 3.40 + 3.60 + 3.80 + 4.00}{14}$
 $\frac{40.00}{14} = 2.857$



By eqn (1) and (2)

$$\ln m + \ln \theta = \ln A - \frac{hc}{2.303} (\lambda kT)^{-1}$$

$$\ln \theta = \ln B - \frac{hc}{2.303} (\lambda kT)^{-1} \quad \text{where } \ln B = \ln \left(\frac{A}{m} \right)$$

The graph plotted b/w $\ln \theta \propto \frac{1}{T}$ is straight line & its slope is given by $\frac{hc}{2.303 \lambda}$

The planck constant $h = \frac{2.303 \lambda k}{c} \times \text{slope of line}$

Temperature of filament of bulb

let R_T be the resistance of the filament of bulb of temp. T and R_0 at room temp. Then

$$\frac{R_T}{R_0} = \left(\frac{T}{T_0} \right)^{1.2}$$

$$T = T_0 \left(\frac{R_T}{R_0} \right)^{0.833}$$

$R_0 \rightarrow$ measured at mv

$R_T \rightarrow$ measured resistance at V_0 mode.

Observation Table:-

Resistance of filament at room temp.

(in VA mode the stopping potential for the filter

are-

for red filter $V_3 = 3V$

green filter $V_2 = 2.20V$

Blue filter $V_1 = 1.98V$

electronic charge $(e) = 1.6 \times 10^{-19} C$

speed of light $(c) = 3 \times 10^8 m/sec$

(iii) for third and first filter

$$h_3 = \frac{c(V_3 - V_2)d_1d_3}{c(d_1 - d_2)}$$

$$h_3 = \frac{1.6 \times 10^{-19} (V_3 - V_1) 6143 \times 4865 \times 10^{-34}}{3000 \times 1278}$$

$$h_3 = 12.47 (V_3 - V_1) \times 10^{-34} \text{ Jsec}$$

$$h_3 = 12.47 (3 - 1.98) \times 10^{-34}$$

$$\boxed{h_3 = 12.71 \times 10^{-34} \text{ J-sec}}$$

Mean value of Planck Constant

$$h = \frac{h_1 + h_2 + h_3}{3}$$

$$\boxed{h = 11.96 \times 10^{-34} \text{ J-sec}}$$

$$\begin{aligned} \text{Percentage Error} &= \frac{\text{Experimental value} - \text{Standard value}}{\text{Standard value}} \times 100\% \\ &= 44.69\% \end{aligned}$$

wavelength of Blue (1st) filter $\lambda_1 = 643 \times 10^{-10} \pm 2\% \text{ m}$
 wavelength of green (2nd) filter $\lambda_2 = 5645 \times 10^{-10} \pm 2\% \text{ m}$
 wavelength of Red (3rd) filter $\lambda_3 = 4865 \times 10^{-10} \pm 2\% \text{ m}$

Planck constant of first and second filter

$$h_1 = \frac{e(V_2 - V_1)\lambda_1\lambda_2}{c(\lambda_1 - \lambda_2)}$$

Similarly, for h_2 & h_3 .

Observation Table :-

For Blue colour


	voltage (v)	current (μA)
1.	2.20	0.4
2	2.40	2.4
3	2.60	3.4
4	2.80	5.0
5	3.00	6.8
6	3.20	9.0
7	3.40	11.0
8	3.60	13.6
9	3.80	16.6
10	4.00	20.6

For Green fielder

X-axis

Y-axis

cm

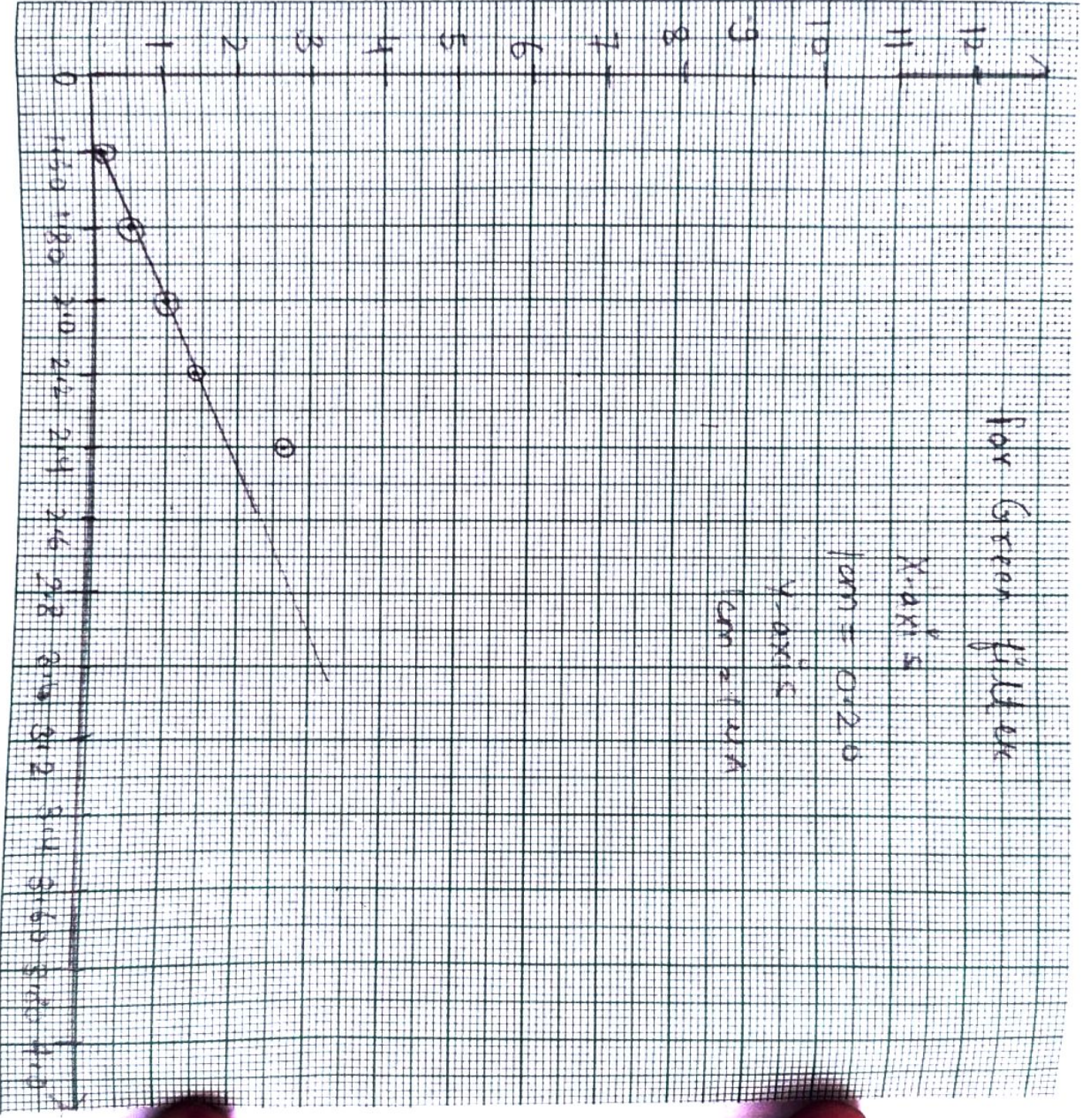

for green colour		for red filter		
Voltage (V)	Current (mA)	S.No.	Voltage (V)	Current
1.60	0.1	1	1.60	0.4
1.80	0.4	2	1.80	0.5
2.00	1.0	3	2.0	1.1
2.20	1.6	4	2.20	1.9
2.40	2.6	5	2.40	2.4
2.60	3.6	6	2.60	3.6
2.80	5.2	7	2.80	4.6
3.00	6.8	8	3.00	7.4
3.20	9.2	9	3.20	8.6
3.40	10.8	10	3.40	11.2
3.60	14.0	11	3.60	13.6
3.80	16.6	12	3.80	16.8
4.00	20.0	13	4.00	20.8

Result:- Theoretical value of Planck constant is $h_T = 6.65 \times 10^{-34}$ J-sec.


Experimental value of Planck's constant is

$$h_e = 11.96 \times 10^{-34} \text{ J-sec.}$$


Percentage error in the value as given as

$$\% \text{ error} = 44.69\%$$


Photo cell

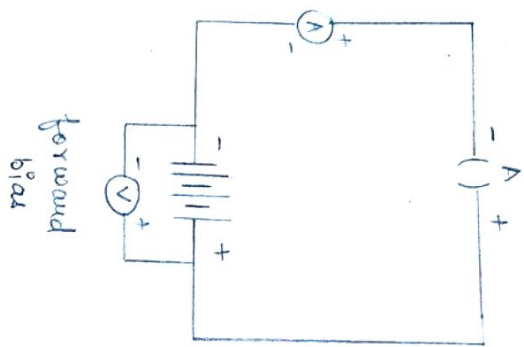

forward bias

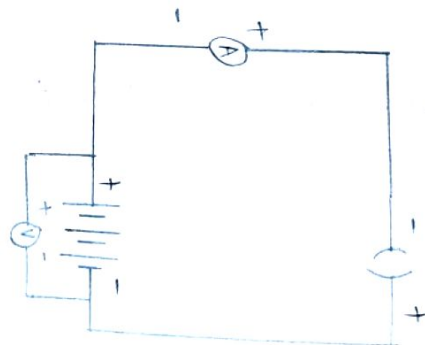

Reverse bias

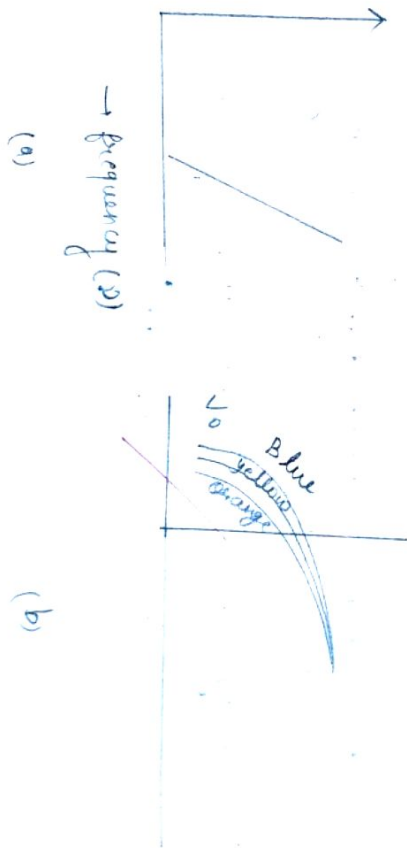

(a)

(b)

Aim:- To determine the Planck constant with the help of photocell.

Apparatus:- Photocell, wooden box to photocell, blue, green and orange filter etc.

Theory:- It is well known that light has dual nature when light properties propagate from one point to another, it behaves like an electromagnetic wave but when it interacts with matter, it behaves like a particle or quanta known as photon

$$E = h\nu$$

where h = Planck's constant

Now, from Einstein's photocell electric equation

$$\frac{1}{2} m v^2 = eV_0 = h\nu - h\nu_0$$

$$V_0 = V_0 = \left(\frac{h\nu}{e}\right) - \left(\frac{h\nu_0}{e}\right) \quad \text{--- (1)}$$

where, m = mass of electron

ν_0 = threshold frequency

$V_0 = V$ = velocity of photoelectron

e = electric charge

Slope of equation (1) $h = e \tan \theta$

Make connection according to figure with light source and align filter properly.

First place blue filter at the stand such that the light of photocell falls on the lamp while passing through the blue filter.

Teacher's Signature : _____

Calculations :-

$$c = 1.6 \times 10^8 \text{ m/sec} \quad c = 3 \times 10^8 \text{ m/sec}$$

wavelength of orange filter $\lambda_o = 5400 \times 10^{-8} \text{ cm}$

wavelength of blue filter $\lambda_B = 5700 \times 10^{-8} \text{ cm}$

wavelength of green filter $\lambda_g = 5200 \times 10^{-8} \text{ cm}$

frequency of blue filter (ν_B) = $\frac{c}{\lambda_B} = 58.8 \times 10^{13} \text{ sec}^{-1}$

frequency of green filter (ν_g) = $\frac{c}{\lambda_g} = 57.6 \times 10^{13} \text{ sec}^{-1}$

frequency of orange filter (ν_o) = $\frac{c}{\lambda_o} = 55.5 \times 10^{13} \text{ sec}^{-1}$

from graph, slope of straight line between stopping potential and frequency $\tan \theta = h/e$

$$h = e \tan \theta$$

$$\tan \theta = \frac{40 \times 10^{-3}}{1.2 \times 10^{13}} = 33.33 \times 10^{-16}$$

$$\text{Now, } h = e \tan \theta \Rightarrow \tan \theta = \frac{40 \times 10^{-3}}{1.2 \times 10^{13}} = 33.33 \times 10^{-16}$$

$$\text{Now, } h = e \tan \theta = 1.6 \times 10^{-19} \times 33.33 \times 10^{-16}$$

$$h = 5.33 \times 10^{-34} \text{ J-sec}$$

$$\text{Percentage error} = \frac{\text{Practical value} - \text{Standard value}}{\text{Practical value}} \times 100 \%$$

$$= \frac{1.29}{662} \times 100 \%$$

$$= 0.1948 \times 100 \%$$

$$= 19.48 \%$$


the current in ammeter doubles 400 μ A for blue filter.


Now increase the voltage gradually & note down the corresponding reading of current in μ A.
Similarly note down reading of $V_{\text{and } I}$ for R.B.
Repeat the steps for green and orange light.

Observation Table :-

Blue filter			
Forward Bias	Reverse Bias		
Voltage (V)	Current (μ A)	Voltage (mV)	Current (μ A)
0	480	0	480
0.1	490	20	440
0.2	500	40	420
		60	400
		80	390
		100	380
		120	350
		140	330
		180	300
		200	280
		220	250
		240	200
		260	180
		280	150
		300	120
		320	90

Teacher's Signature : _____

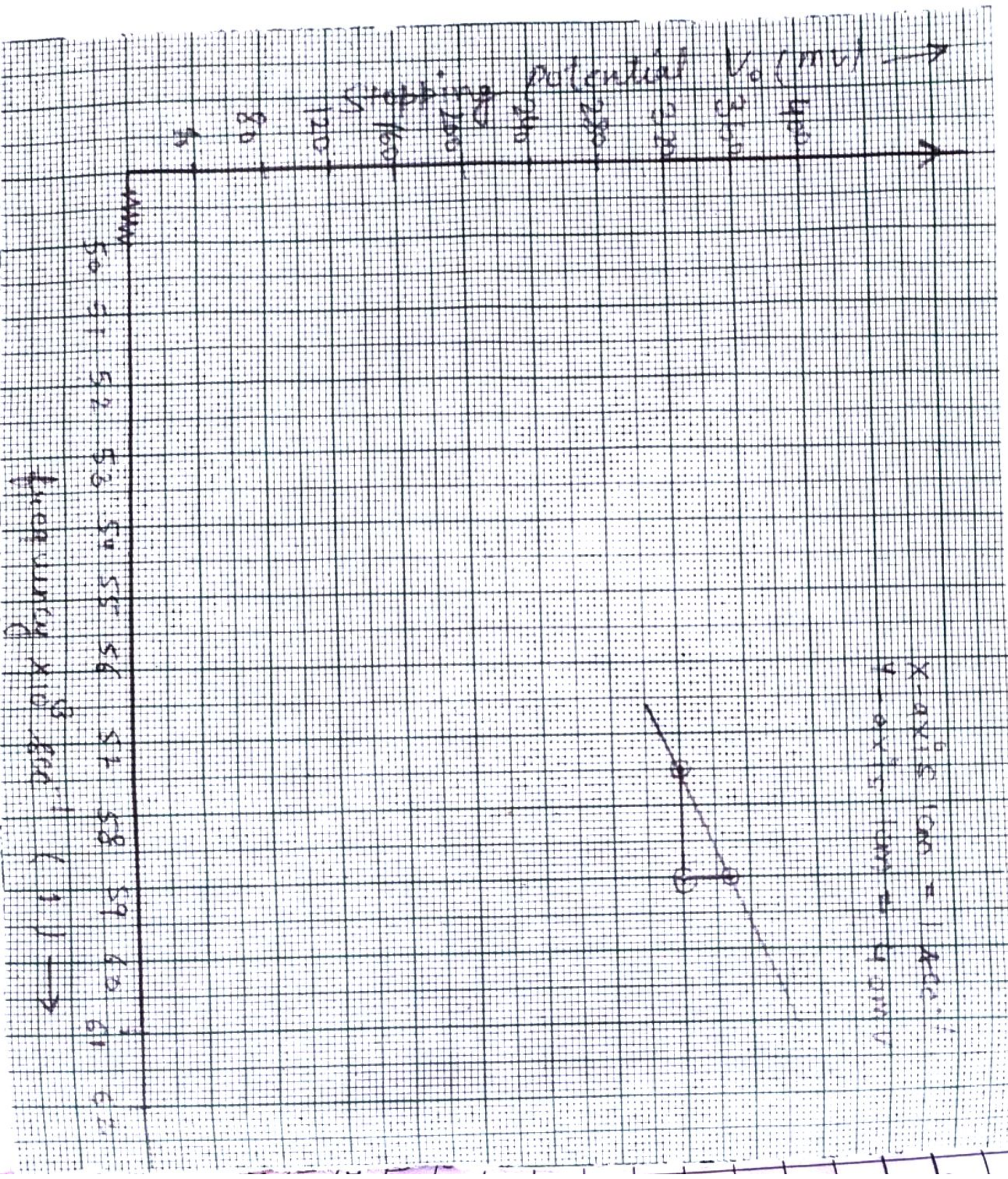

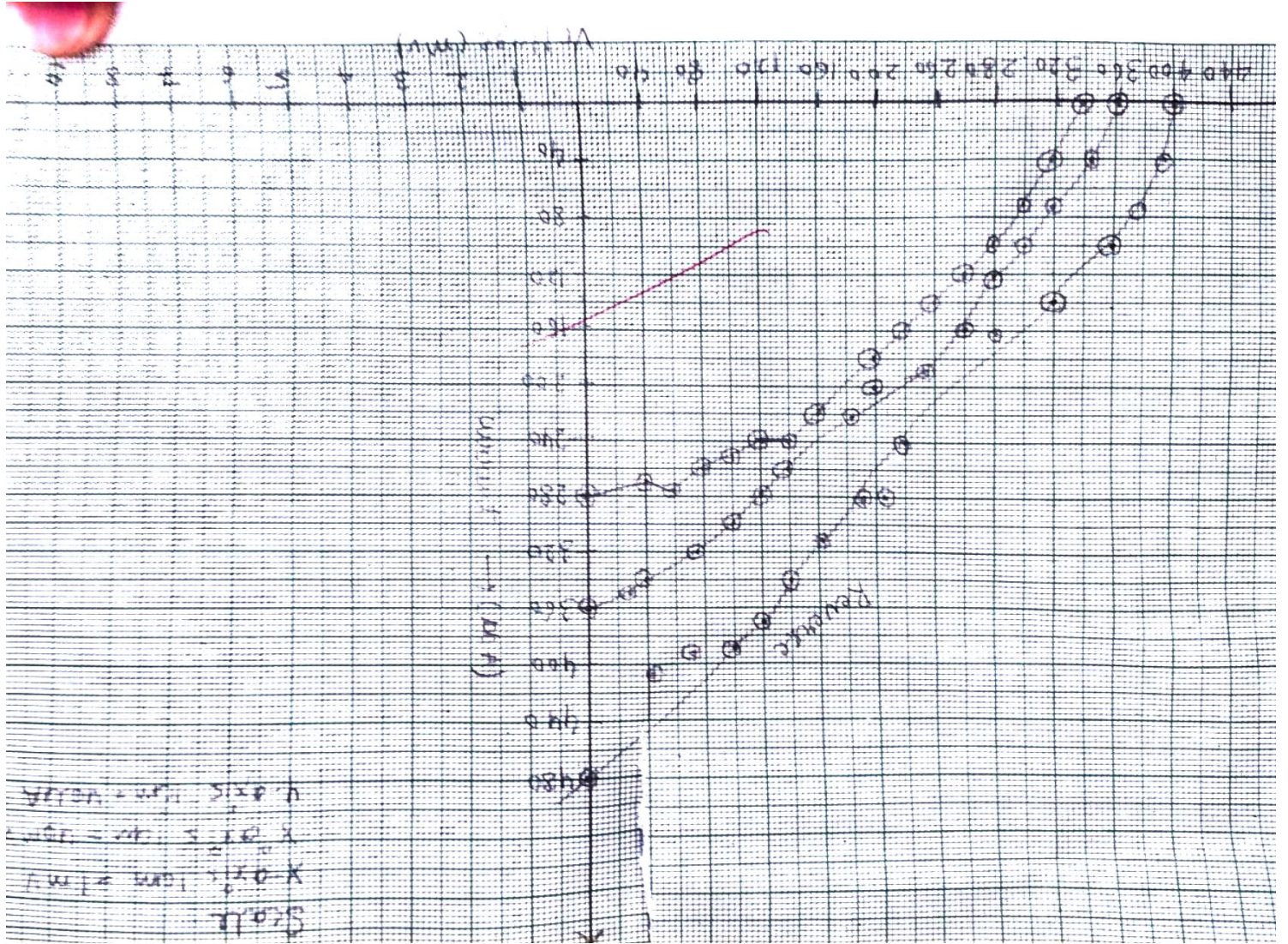

1	0	280	0	280
2	1	360	20	270
3	2	430	40	260
4	3	500	60	250
5			80	240
6			100	280
7			120	220
8			140	210
9			160	190
10			180	170
11			200	140
12			220	120
13			240	100
14			260	70
15			280	40
16			300	0

Result :-

Theoretical value of Planck's constant is

$$6.62 \times 10^{-34} \text{ J-s}$$

Practical value of Planck's constant is

$$5.22 \times 10^{-34} \text{ Joule-sec.}$$

Percentage error = 19.48%

Filter	Frequency (sec ⁻¹)	Stopping potential (eV)
Blue	360	5.3×10^{-13}
Green	320	5.76×10^{-13}
Orange	300	5.5×10^{-13}

Teacher's Signature : _____

W
10/11/19